

## Network Theory

1. Circuit Theory Analysis - Mesh Analysis and Nodal Analysis.
2. Star-Delta Transformation
3. Network Theorem - Superposition Theorem, Norton Theorem and Maximum Power transfer Theorem.


→ Kirchoff's Voltage Law: The algebraic sum of voltage drop in any closed path in a specified direction is equal to 0.

→ Kirchoff's Current Law: The algebraic sum of incoming and outgoing current in a junction is 0.
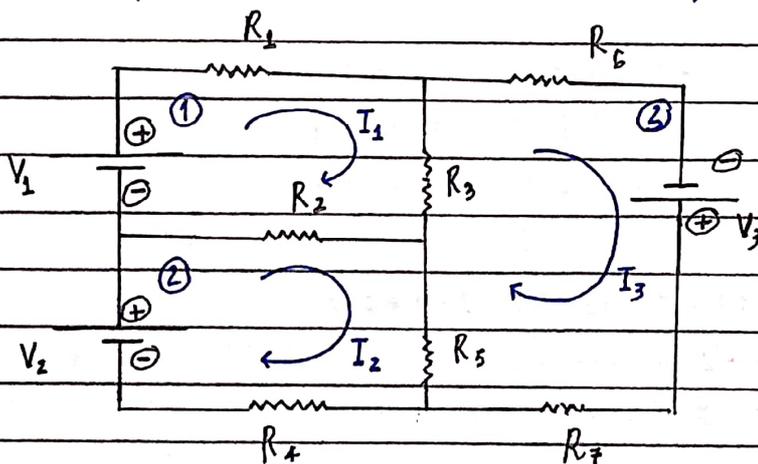
### 1. Mesh Analysis:

Mesh or loop analysis is based on Kirchoff's voltage law, it is used to find out unknown current, voltage in the mesh.

In this method, each mesh is assigned a separate mesh current and KVL is applied to write the mesh equation.



$$R_6 I_3 + R_7 I_3 + R_5 (I_3 - I_2) + R_3 (I_3 - I_1) = 0$$

$$-I_1 R_3 - I_2 R_5 + I_3 (R_3 + R_5 + R_6 + R_7) = V_3 \quad \text{--- (3)}$$


$$I_1 R_1 + R_3 (I_1 - I_3) + R_2 (I_1 - I_2) = V_1$$

$$I_1 (R_1 + R_2 + R_3) - I_2 R_2 - I_3 R_3 = V_1 \quad \text{--- (1)}$$

$$R_2 (I_2 - I_1) + R_5 (I_2 - I_3) + R_4 I_2 = V_2$$

$$-R_2 I_1 + I_2 (R_2 + R_5 + R_4) - I_3 R_5 = V_2 \quad \text{--- (2)}$$

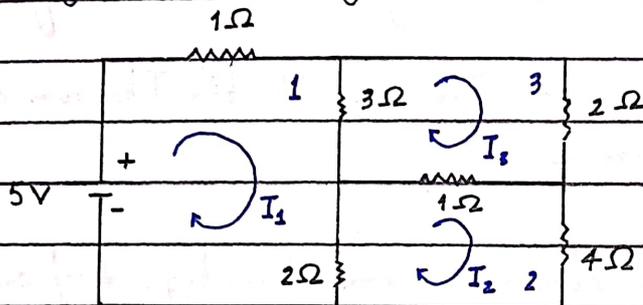Q. Find the current  $I_1$ ,  $I_2$  and  $I_3$  of the given network using mesh analysis.



$$5I_1 + 3(I_1 - I_3) + 2(I_1 - I_2) = 5$$

$$I_1(10) - I_2 \cdot 2 + 5I_1 = 5$$

$$10I_1 - 2I_2 - 3I_3 = 5 \quad \text{--- (1)}$$

$$3(I_3 - I_1) + 1(I_3 - I_2) + 2I_3 = 0$$

$$6I_3 - 3I_1 - I_2 = 0 \quad \text{--- (3)}$$

$$1(I_2 - I_3) + 4I_2 + 2(I_2 - I_1) = 0$$

$$-2I_1 + 7I_2 - I_3 = 0 \quad \text{--- (2)}$$

Arranging the mesh equations into matrix form and using Cramer's rule.

$$[I][R] = [V]$$

$$\Rightarrow \begin{bmatrix} 6 & -2 & -3 \\ -2 & 7 & -1 \\ -3 & -1 & 6 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{aligned} \therefore \Delta &= 6(42 - 1) + 2(-12 + 3) - 3(2 + 21) \\ &= 6(41) + 2(-15) - 3(23) \\ &= 246 - 30 - 69 \\ &= 147 \end{aligned}$$

$$\therefore \begin{bmatrix} 5 & -2 & -3 \\ 0 & 7 & -1 \\ 0 & -1 & 6 \end{bmatrix}, \Delta_1 = 5(41) + 2(0) - 3(0) = 205$$

$$\Delta_2 = \begin{vmatrix} 6 & 5 & -3 \\ -2 & 0 & -1 \\ -3 & 0 & 6 \end{vmatrix} = 6(0) - 5(-15) - 3(0) = +75$$


$$\Delta_3 = \begin{vmatrix} 6 & -2 & 5 \\ -2 & 7 & 0 \\ -3 & -1 & 0 \end{vmatrix} = 6(0) + 2(0) - 5(23) = -115$$

$$\Rightarrow I_1 = \frac{\Delta_1}{\Delta} = \frac{205}{147} = 1.39 \text{ A}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{75}{147} = 0.51 \text{ A}$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{-115}{147} = -0.78 \text{ A ans}$$

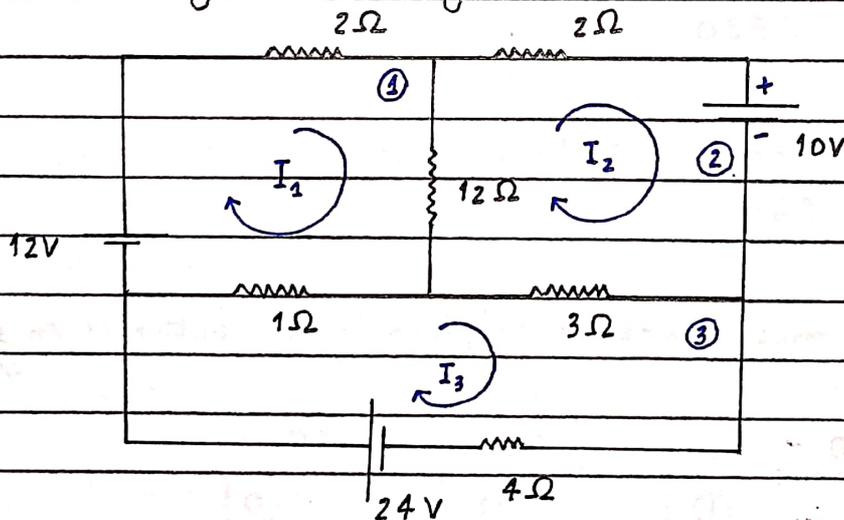Q. Determine the branch current in  $4\Omega$  resistor in the given network using mesh analysis.



$$\therefore 2I_1 + 12(I_1 - I_2) + 1(I_1 - I_3) = 12$$

$$15I_1 - 12I_2 - I_3 = 12 \quad \text{--- (1)}$$

$$2I_2 + 12(I_2 - I_1) + 3(I_2 - I_3) = -10$$

$$-12I_1 + 17I_2 - 3I_3 = -10 \quad \text{--- (2)}$$

$$1(I_3 - I_1) + 3(I_3 - I_2) + 4I_3 = 24$$

$$-I_1 - 3I_2 + 8I_3 = 24 \quad \text{--- (3)}$$

Arranging mesh equations into matrix form and using crammer's rule.

$$\therefore [R][I] = [V]$$

$$\begin{bmatrix} 15 & -12 & -1 \\ -12 & 17 & -3 \\ -1 & -8 & 8 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 12 \\ -10 \\ 24 \end{bmatrix}$$

$$\therefore \Delta = \begin{vmatrix} 15 & -12 & -1 \\ -12 & 17 & -3 \\ -1 & -3 & 8 \end{vmatrix} = 15(17 \cdot 8 - 9) + 12(-96 - 3) - 1(36 + 12)$$


$$\therefore \Delta = 664$$

$$\Delta_3 = \begin{vmatrix} 15 & -12 & 12 \\ -12 & 17 & -10 \\ -1 & -3 & 24 \end{vmatrix} = 15(17 \cdot 24 - 30) + 12(-12 \cdot 24 - 10) + 12(36 + 17)$$

$$\Delta_3 = 2730$$

$$\Rightarrow I_3 = \frac{2730}{664} = 4.11 \text{ A ans}$$

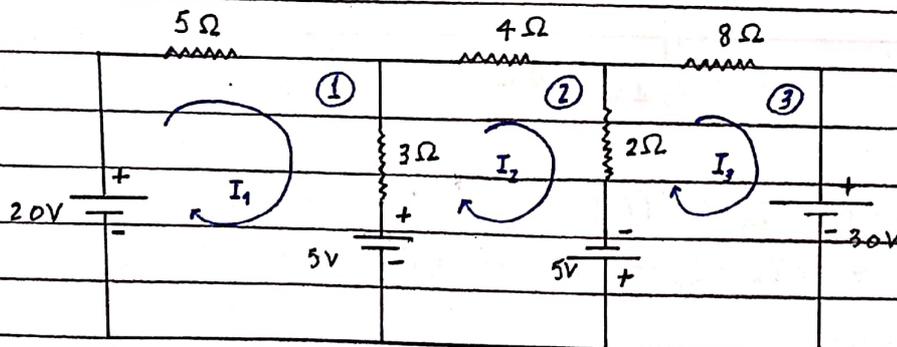Q. Determine the mesh current supplied by the batteries in given network.



$$5I_1 + 3(I_1 - I_2) = 20 - 5$$

$$8I_1 - 3I_2 = 15 \quad \text{--- (1)}$$

$$4I_2 + 3(I_2 - I_1) + 2(I_2 - I_3) = 5 + 5 + 5$$

$$-3I_1 + 9I_2 - 2I_3 = 15 \quad \text{--- (2)}$$

$$8I_3 + 2(I_3 - I_2) = -30 - 5$$

$$-2I_2 + 20I_3 = -35 \quad \text{--- (3)}$$

Arranging the mesh equations into matrix form and using Cramer's Rule.

$$\begin{bmatrix} 8 & -3 & 0 \\ -3 & 9 & -2 \\ 0 & -2 & 10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 15 \\ 15 \\ -35 \end{bmatrix}$$

$$\begin{aligned} \therefore \Delta &= 8(90-4) + 3(-30) \\ &= 8(86) - 90 \\ &= 598 \text{ ans} \end{aligned}$$

$$\Delta_1 = \begin{vmatrix} 15 & -3 & 0 \\ 15 & 9 & -2 \\ -35 & -2 & 10 \end{vmatrix} = 15(86) + 3(150-70) = 1050$$

$$\begin{aligned} \Delta_2 &= \begin{vmatrix} 8 & 15 & 0 \\ -3 & 15 & -2 \\ 0 & -35 & 10 \end{vmatrix} = 8(150-70) - 15(-30) \\ &= 8(80) + 450 \\ &= 640 + 450 = 1090 \end{aligned}$$


$$\begin{aligned} \Delta_3 &= \begin{vmatrix} 8 & -35 & 15 \\ -3 & 9 & 15 \\ 0 & -2 & -35 \end{vmatrix} = 8(9(-35)-30) + 35(3 \times 35) + 15(6) \\ &= 1005 \end{aligned}$$

$$\Rightarrow I_1 = \frac{\Delta_1}{\Delta} = \frac{1050}{598} = 1.755 \text{ A}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{1090}{598} = 1.822 \text{ A}$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{1005}{598} = 1.68 \text{ A} \quad \underline{\underline{\text{ans}}}$$

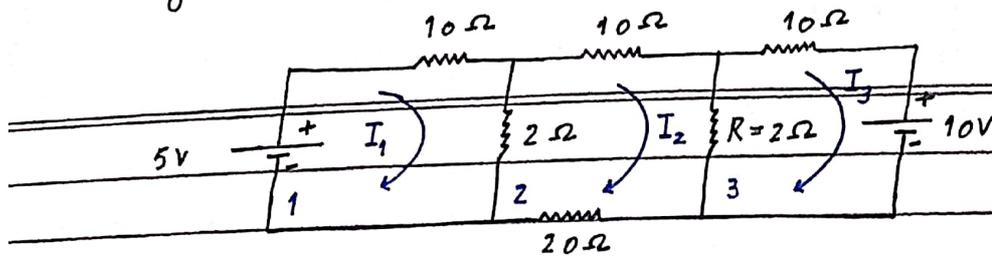Q. Find the voltage across the resistor using Mesh Analysis.



Applying mesh analysis in mesh 1

$$-10I_1 - 2(I_1 - I_2) + 5 = 0$$

$$-12I_1 + 2I_2 = -5$$

$$12I_1 - 2I_2 = 5 \quad \text{--- (1)}$$

Applying mesh analysis in mesh 2

$$-10I_2 - 2(I_2 - I_3) - 20I_2 - 2(I_2 - I_1) = 0$$

$$-34I_2 + 2I_3 + 2I_1 = 0$$

$$I_1 - 17I_2 + I_3 = 0 \quad \text{--- (2)}$$

Applying mesh analysis in mesh 3

$$-10 - 2(I_3 - I_2) - 10I_3 = 0$$

$$+2I_2 - 12I_3 = 10$$

$$I_2 - 6I_3 = 5 \quad \text{--- (3)}$$

Arranging mesh equations into matrix form and applying crammer's rule.

$$\therefore \begin{bmatrix} 12 & -2 & 0 \\ 1 & -17 & 1 \\ 0 & 1 & -6 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 5 \end{bmatrix}$$

$$\therefore \Delta = \begin{vmatrix} 12 & -2 & 0 \\ 1 & -17 & 1 \\ 0 & 1 & -6 \end{vmatrix} = 12(17(6) - 1) + 2(-6) \\ 12(101) - 12 \\ = 1200.$$

$$\Delta_2 = \begin{vmatrix} 12 & 5 & 0 \\ 1 & 0 & 1 \\ 0 & 5 & -6 \end{vmatrix} = 12(-5) - 5(-6) = -60 + 30 = -30$$

$$\Delta_3 = \begin{vmatrix} 12 & -2 & 5 \\ 1 & -17 & 0 \\ 0 & 1 & 5 \end{vmatrix} = 12((-17)(5)) + 2(5) + 5(1) = -1005$$

$$\therefore I_2 = \frac{\Delta_2}{\Delta} = \frac{-30}{1200} = -0.025$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{-1005}{1200} = -0.8375$$

$\therefore$  The current through  $R = 2 \Omega$ ;

$$I_{2\Omega} = I_2 - I_3 \\ = (-0.025) - (-0.8375)$$

$$I_{2\Omega} = 0.8125 \text{ A ans.}$$

$\Rightarrow$  Voltage across  $2 \Omega$  resistor;

$$V_{2\Omega} = I_{2\Omega} \times 2 \\ = 0.8125 \times 2$$

$$V_{2\Omega} = 1.625 \text{ V Ans.}$$


H Nodal Analysis (Based on KCL)

Nodal Analysis is based on KCL, in this method we define the voltage across each node as an independent.


For the application every node junction in the network where three or more branches meet is regarded as a node. One of these is regarded as a reference node or zero potential node.

Hence, the no. of simultaneous equations to be solved

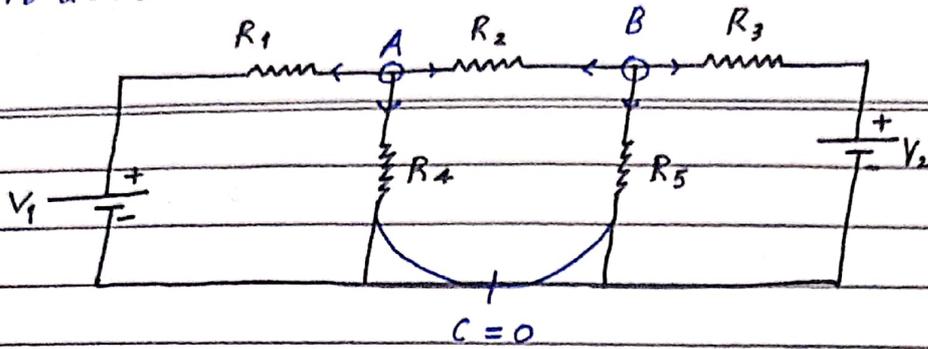becomes  $(n-1)$  where  $n$  is the no. of independent nodes.



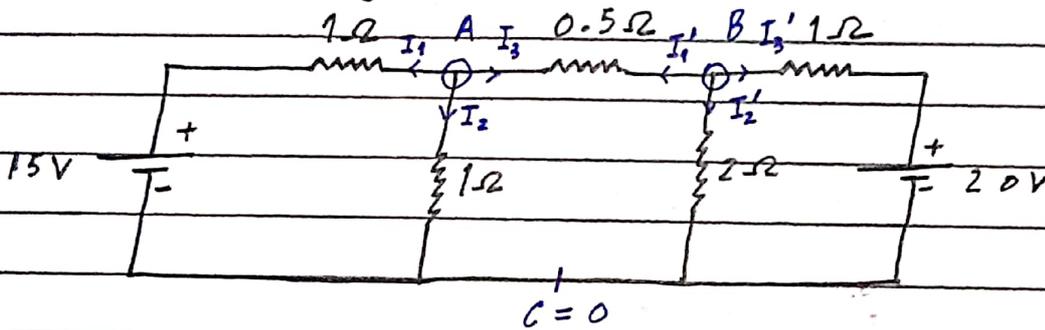Q. Find the branch currents of the given network using nodal analysis.



Let 'A' and 'B' be two node junctions and 'C' be the reference node.

Applying KCL for node A

$$\frac{V_A - 15}{1} + \frac{V_A - 0}{1} + \frac{V_A - V_B}{0.5} = 0$$

$$\therefore 2V_A - 15 + 2V_A - 2V_B = 0$$

$$4V_A - 2V_B = 15 \quad \text{--- (1)}$$

Now, applying KCL for node B

$$\frac{V_B - 20}{1} + \frac{V_B - 0}{2} + \frac{V_B - V_A}{0.5} = 0$$

$$\frac{3}{2}V_B - 20 + 2V_B - 2V_A = 0$$

$$7V_B - 4V_A = 40$$

$$7V_B - 4V_A = 40 \quad \text{--- (2)}$$

Adding ① and ②

$$\therefore 4V_A - 2V_B = 15$$

$$7V_B - 4V_A = 40$$

$$\underline{5V_B = 55}$$

$$\therefore V_B = \frac{55}{5} = 11V$$

$$\Rightarrow 4V_A - 22 = 15$$

$$V_A = 9.25V$$

$$\therefore I_1 = 9.25 - 15 = -5.75A$$

$$I_2 = 9.25A$$

$$I_3 = (9.25 - 11)2 = -3.5A$$


$$I_2' = 5.5A$$

$$I_3' = 11 - 20 = -9A$$

$$I_1' = (11 - 9.25) \times 2 = 3.5$$

$$I_{0.5\Omega} = 3.5 - (-3.5) = 7A \quad \text{Ans.}$$

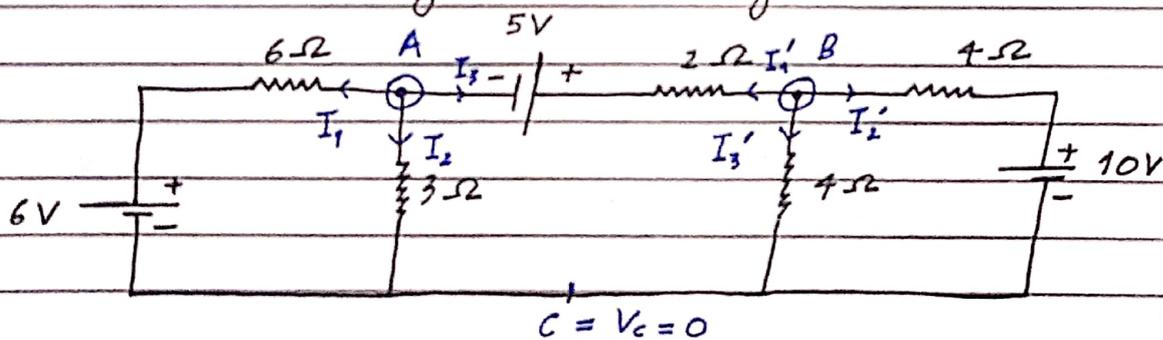Q. Find the branch current in the given network using nodal analysis.



Let 'A' and 'B' be two node junctions with potential ' $V_A$ ' and ' $V_B$ ' respectively and 'C' be reference potential node.

$\therefore$  Applying KCL on node 'A'

$$\frac{V_A - 6}{6} + \frac{V_A - 0}{3} + \frac{V_A + 5 - V_B}{2} = 0$$

$$V_A - 6 + 2V_A + 3V_A + 15 - 3V_B = 0$$

$$6V_A - 3V_B = -9$$

$$2V_A - V_B = -3 \quad \text{--- (1)}$$

Now, applying KCL on node 'B':

$$\frac{V_B - 5 - V_A}{2} + \frac{V_B}{4} + \frac{V_B - 10}{4} = 0$$

$$2V_B - 10 - 2V_A + 2V_B - 10 = 0$$

$$4V_B - 2V_A = 20 \quad \text{--- (2)}$$

∴ Adding (1) and (2)

$$\cancel{2V_A} - V_B = -3$$

$$\cancel{4V_B} - \cancel{2V_A} = 20$$

$$3V_B = 17$$

$$V_B = \frac{17}{3} = 5.66 \text{ V}$$

$$\therefore 2V_A = -3 + V_B$$

$$V_A = \frac{-3 + 5.66}{2} = 1.33 \text{ V}$$

$$\Rightarrow I_1 = \frac{V_A - 6}{6} = \frac{1.33 - 6}{6} = -0.77 \text{ A}$$

$$I_2 = \frac{V_A}{3} = \frac{1.33}{3} = 0.44 \text{ A}$$

$$I_3 = \frac{V_A + 5 - V_B}{2} = \frac{1.33 + 5 - 5.66}{2} = 0.335 \text{ A}$$


$$I_1' = \frac{V_B - 5 - V_A}{2} = \frac{5.66 - 5 - 1.33}{2} = -0.335$$

$$I_2' = \frac{V_B - 10}{4} = \frac{5.66 - 10}{4} = -1.085 \text{ A}$$

$$I_3' = \frac{V_B}{4} = \frac{5.66}{4} = 1.415 \text{ A}$$

$$\therefore I_{AB} = I_1 - I_1' = 0.335 - (-0.335) = 0.67 \text{ Ans.}$$

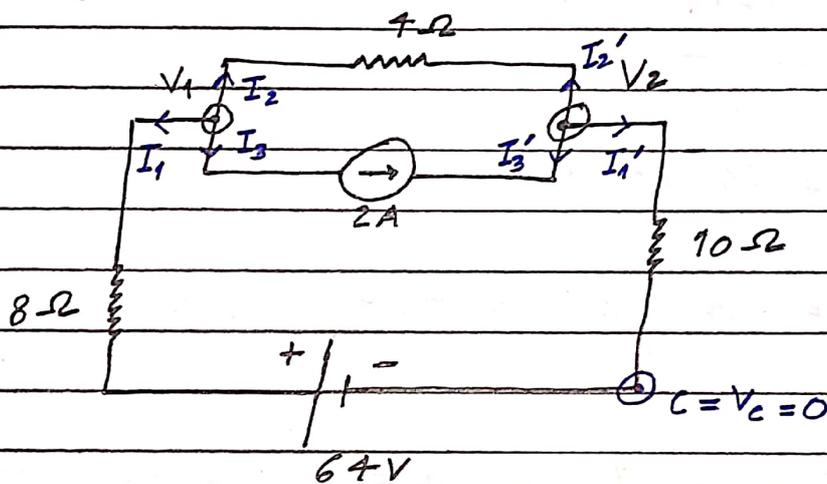Q. Using Nodal Analysis, calculate  $V_1$  and  $V_2$ .



Let 'C' be the reference node.

$$\begin{array}{r} 2 \mid 10.4 \\ \hline 2 \mid 5 \\ \hline 5 \mid \end{array}$$

Applying KCL on  $V_1$ .

$$\frac{V_1 - 64}{8} + \frac{V_1 - V_2}{4} + 2 = 0$$

$$V_1 - 64 + 2V_1 - 2V_2 = -16$$

$$3V_1 - 2V_2 = 48 \quad \text{--- (1)}$$

Applying KCL on  $V_2$ .

$$\frac{V_2}{10} + \frac{V_2 - V_1}{4} - 2 = 0$$

$$2V_2 + 5V_2 - 5V_1 = 40$$

$$7V_2 - 5V_1 = 40 \quad \text{--- (2)}$$

Multiplying eq ① by 5

$$15V_1 - 10V_2 = 240 \text{ --- ③}$$

Multiplying eq ② by 3

$$21V_2 - 15V_1 = 120 \text{ --- ④}$$

Adding ③ and ④

~~$$15V_1 - 10V_2 = 240$$~~

~~$$21V_2 - 15V_1 = 120$$~~

$$11V_2 = 120$$


$$V_2 = 10.90 \text{ V}$$

and

$$V_1 = \frac{48 + 2V_2}{3} = \frac{48 + 21.81}{3} = 23.27 \text{ V}$$

Ans.

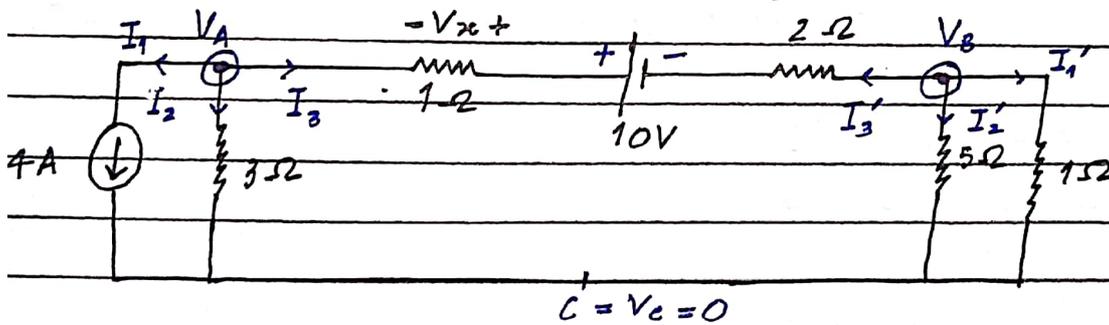Q. Calculate the current through  $5\Omega$  also find  $V_x$ .



Let 'A' and 'B' be two nodes with potentials as ' $V_A$ ' and ' $V_B$ ' respectively.  
'C' be the reference node.

Applying KCL on node 'A'

$$4 + \frac{V_A}{3} + \frac{V_A - 10 - V_B}{3} = 0$$

$$2V_A - V_B = -2 \text{ --- ①}$$

Applying KCL on node 'B'

$$\therefore V_B + \frac{V_B}{5} + \frac{V_B + 10 - V_A}{3} = 0$$

$$15V_B + 3V_B + 5V_B + 50 - 5V_A = 0$$

$$23V_B - 5V_A = -50 \quad \text{--- (2)}$$

$$\therefore \textcircled{1} \times 5 + \textcircled{2} \times 2$$

$$\Rightarrow 10V_A - 5V_B = -10$$

$$+6V_B - 10V_A = -100$$

$$\hline 41V_B = -110$$

$$V_B = \frac{-110}{41} = -2.68 \text{ V}$$

$$\therefore V_A = \frac{-2 + V_B}{2} = -2.34 \text{ V}$$

$$\therefore I_{3\Omega} = \frac{V_B}{5} = \frac{-2.68}{5} = -0.536 \text{ A ans.}$$

$$\text{and } I_3 = \frac{V_A - 10 - V_B}{3} = \frac{-2.34 - 10 + 2.68}{3} = -3.22 \text{ A}$$


$$I_3' = \frac{V_B + 10 - V_A}{3} = \frac{-2.68 + 10 + 2.34}{3} = 3.22 \text{ A}$$

$$I_{1\Omega} = I_3' - I_3$$

$$\therefore I_{1\Omega} = 3.22 - (-3.22) = 6.44 \text{ A}$$


$$\Rightarrow V_x = 1 \times 6.44 = 6.44 \text{ V} \quad \underline{\underline{\text{Ans.}}}$$

# # Star-Delta Transformation

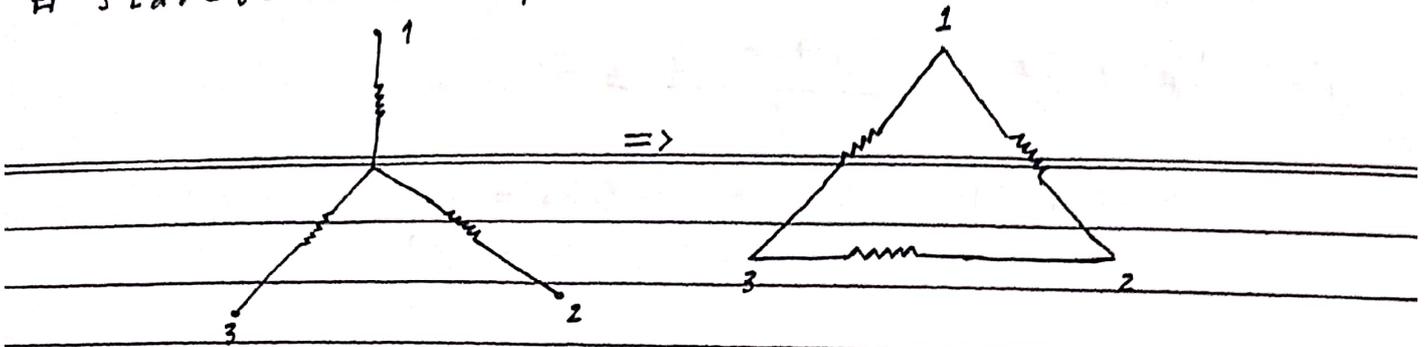

There are some networks in which resistors are neither connected in series nor in parallel such as star-delta networks.

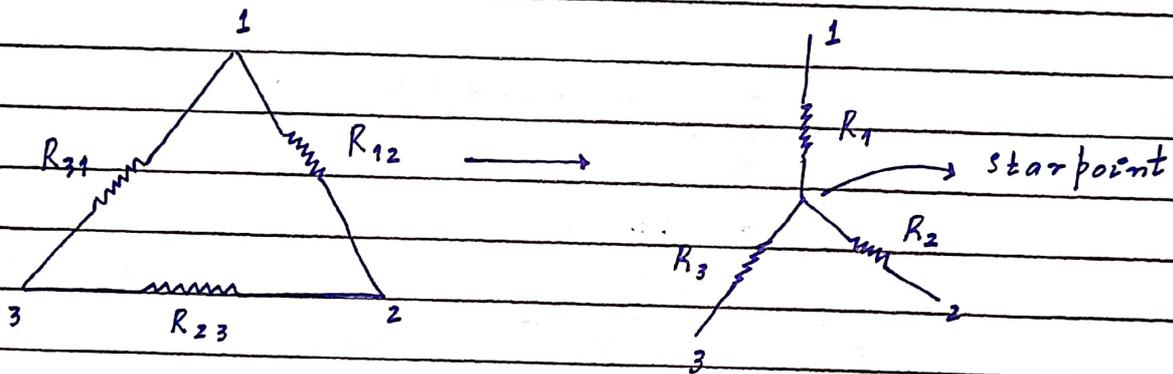In such simulations, it is not possible to simplify the network by series and parallel circuit nodes however such network can be simplified by using star-delta transformation technique.





## → Delta to Star transformation.

Consider three resistors  $R_{12}$ ,  $R_{23}$  and  $R_{31}$  connected in  $\Delta$ , these three given resistors can be replaced by three resistors  $R_1$ ,  $R_2$  and  $R_3$  connected in star.

First we take delta connection between terminal 1 and 2, there are two parallel paths one having resistance  $R_{12}$  and other having resistance  $R_{23} + R_{31}$ . Therefore, the equivalent resistance between one and two:
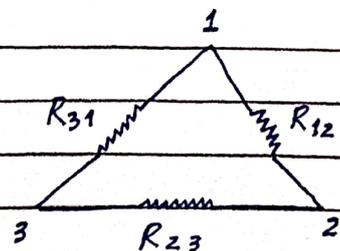
$$\therefore R_{eq} = \frac{R_{12} \parallel (R_{31} + R_{23})}{R_{12} + R_{31} + R_{23}}$$



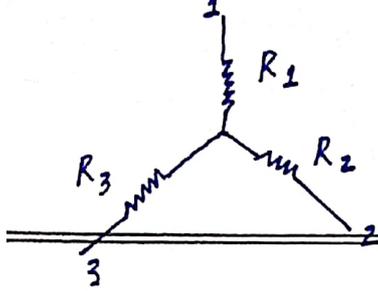

Now, we take star connection, the resistance between same terminal is equal to  $R_1 + R_2$ .

Hence, as the terminal resistance had to be same i.e. resistance between 1 and 2 for star is equal to 1 and 2 for delta.

$$\Rightarrow R_1 + R_2 = \frac{R_{12} (R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}} \quad \text{--- (1)}$$

Similarly,

$$R_2 + R_3 = \frac{R_{23} (R_{31} + R_{12})}{R_{12} + R_{23} + R_{31}} \quad \text{--- (2)}$$

$$\text{and } R_1 + R_3 = \frac{R_{31} (R_{12} + R_{23})}{R_{12} + R_{23} + R_{31}} \quad \text{--- (3)}$$

Now, subtracting (2) from (1)

$$\therefore R_1 - R_3 = \frac{R_{12} R_{23} + R_{12} R_{31} - R_{23} R_{31} - R_{23} R_{12}}{R_{12} + R_{23} + R_{31}}$$

$$R_1 - R_3 = \frac{R_{12} R_{31} - R_{23} R_{31}}{R_{12} + R_{23} + R_{31}}$$

Adding the above result in eq. (3)

$$\therefore 2R_1 = \frac{R_{12} R_{31} + R_{12} R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$\therefore R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}} \quad \text{--- (4)}$$

$$\text{similarly: } R_2 = \frac{R_{12} \cdot R_{23}}{R_{12} + R_{23} + R_{31}} \quad \text{--- (5)} \quad \text{and} \quad R_3 = \frac{R_{31} \cdot R_{23}}{R_{12} + R_{23} + R_{31}} \quad \text{--- (6)}$$

⇒ Star to Delta transformation

Dividing eq (4) and (5)

$$\therefore \frac{R_1}{R_2} = \frac{R_{12} \cdot R_{31}}{R_{12} \cdot R_{23}}$$

$$\frac{R_1}{R_2} = \frac{R_{31}}{R_{23}}$$

$$\therefore R_{31} = \frac{R_1 \times R_{23}}{R_2}$$

and Dividing eq (4) and (6)

$$\frac{R_1}{R_3} = \frac{R_{12}}{R_{23}}$$

$$\therefore R_{12} = \frac{R_1 \cdot R_{23}}{R_3}$$

Substituting the values of  $R_{12}$  and  $R_{31}$  in (4)

$$R_1 = \frac{\frac{R_1 \cdot R_{23}}{R_3} \times \frac{R_1 \cdot R_{23}}{R_2}}{(R_{12} + R_{23} + R_{31})}$$



$$\therefore R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$

$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$R_{31} = R_3 + R_1 + \frac{R_1 R_3}{R_2}$$

Ans.


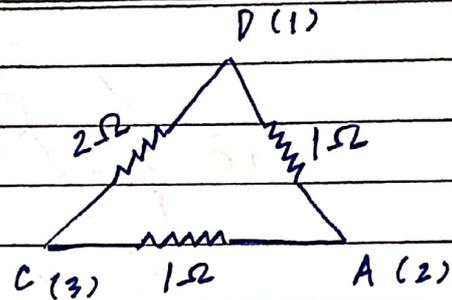
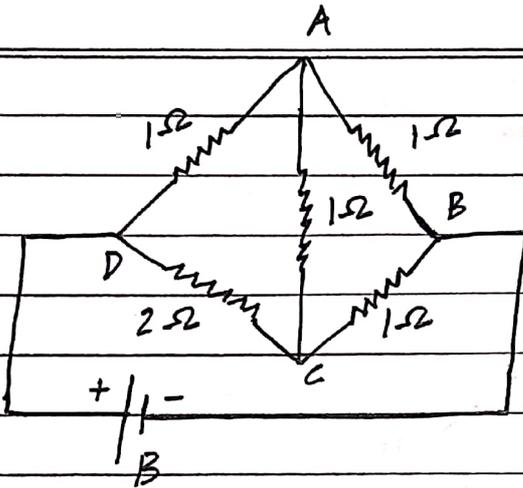
Q. Find the equivalent resistance across the battery terminal of the given network using star, Delta and Delta to star transformation technique.



$$\therefore R_1 = \frac{1 \times 2}{4} = \frac{1}{2} = 0.5 \Omega$$


$$R_2 = \frac{1 \times 1}{4} = 0.25 \Omega$$
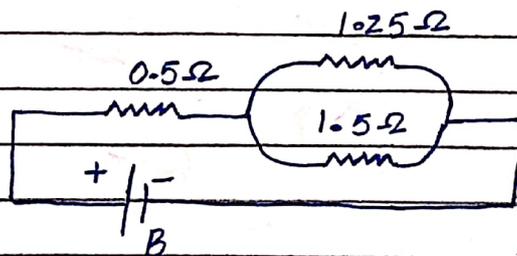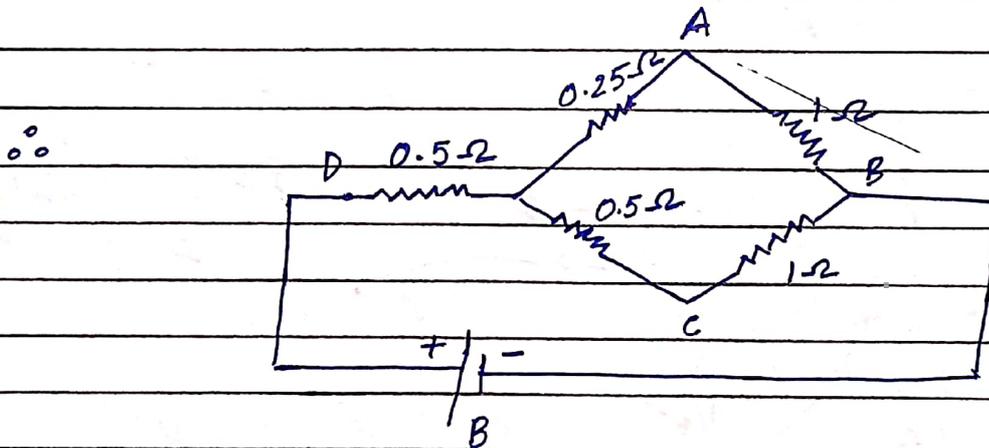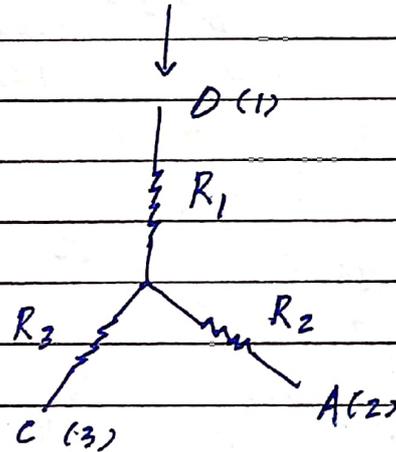
$$R_3 = \frac{1 \times 2}{4} = 0.5 \Omega$$






$$\therefore R_{eq} = 0.5 + (1.25 // 1.5)$$

$$R_{eq} = 1.18 \Omega$$


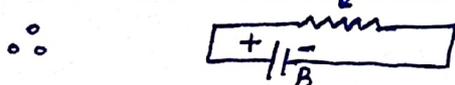


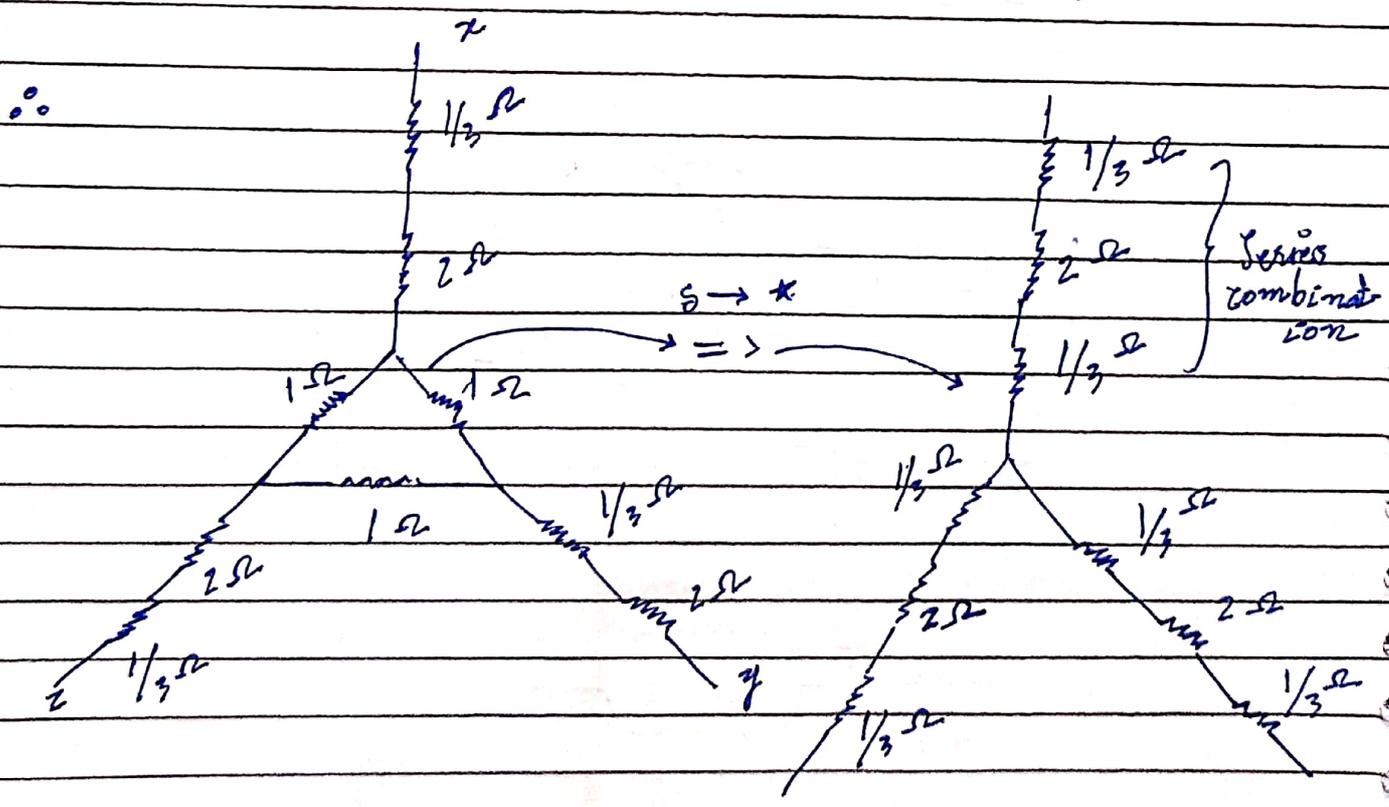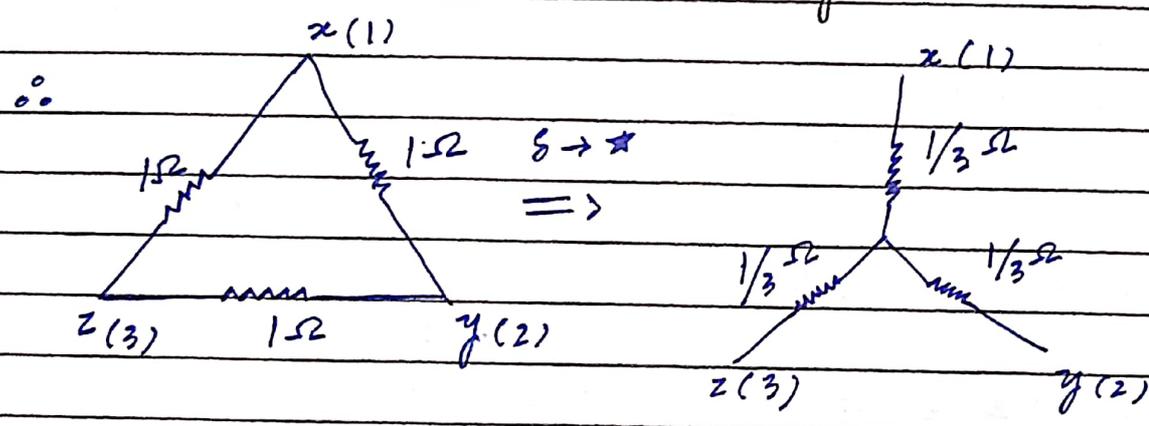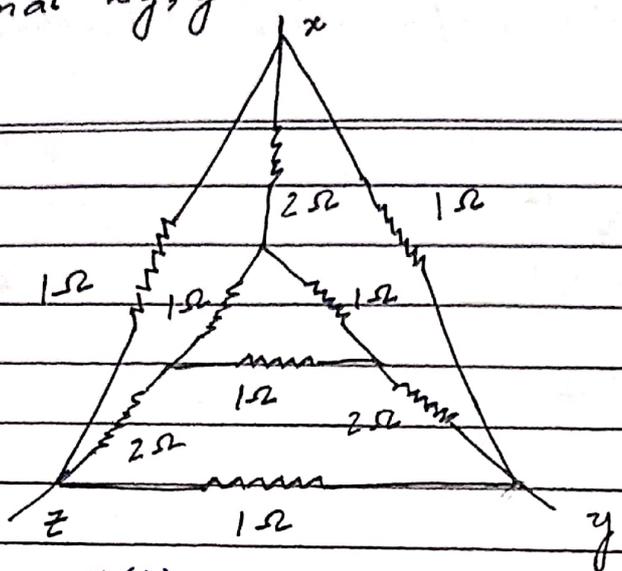Q. Determine the equivalent resistance between the terminal  $xy$ ,  $yz$  and  $zx$ .



$$\frac{2+2}{3}$$

ایسے ظاہر ہے  
کہ  
سر ہے

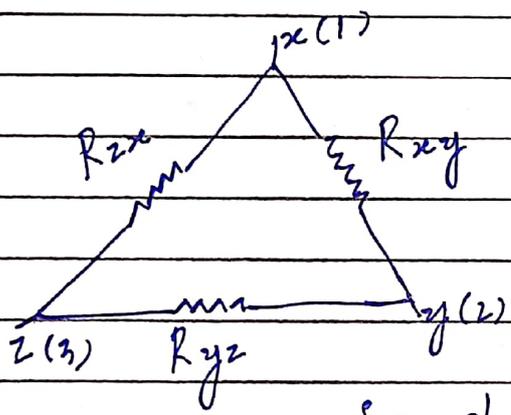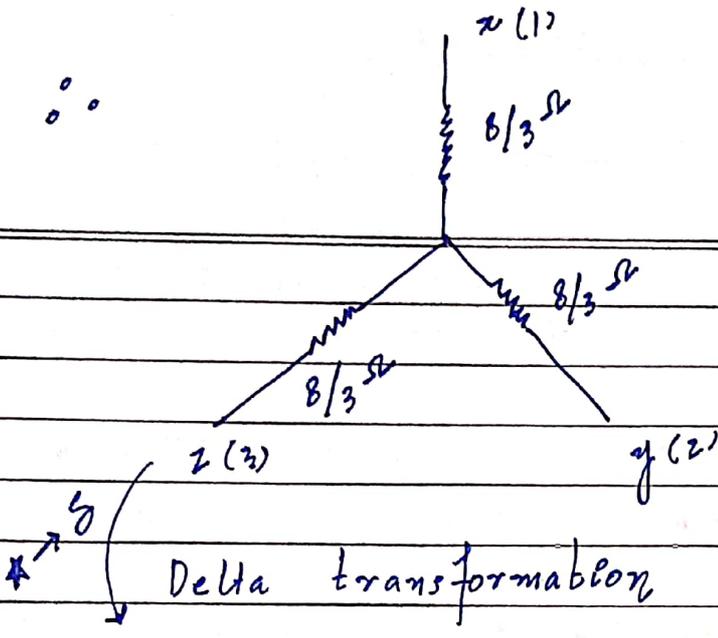


$$\begin{aligned} \therefore R_{xy} &= R_x + R_y + \frac{R_x R_y}{R_z} \\ &= \frac{8}{3} + \frac{8}{3} + \frac{(8/3)(8/3)}{(8/3)} \end{aligned}$$

$$R_{xy} = \frac{8}{3} \times 3 = 8 \Omega$$

Similarly;  $R_{yz} = 8 \Omega$

$$R_{zx} = 8 \Omega$$

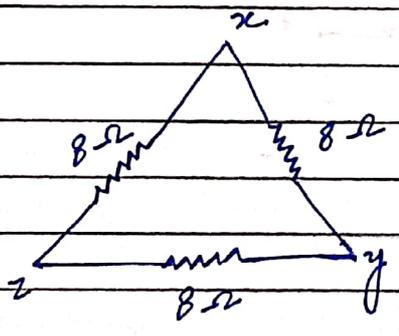
$\therefore$  The given circuit transforms into;



Hence,  
the equivalent resistance  
between terminals xy, yz,  
and zx is 8 Ω.

Ans.


## ≡ Thevenin's Theorem

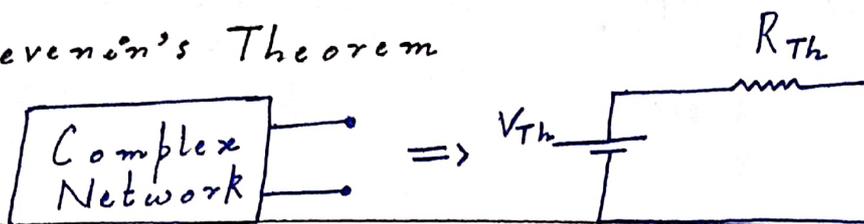


Thevenin's Equivalent Network

Thevenin's Theorem is the most important theorem that can be used for simplification of complicated network.

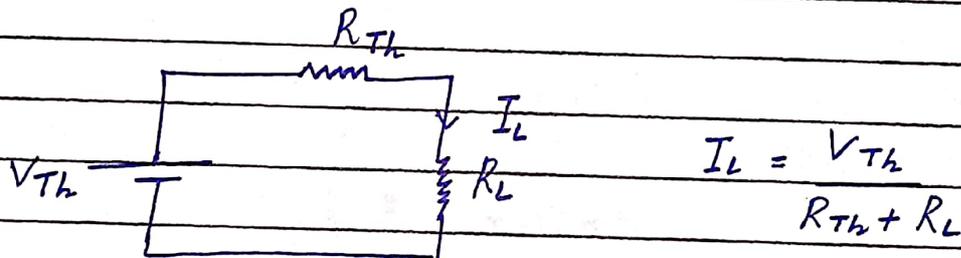Any linear bilateral network having two terminals can be replaced by an equivalent network or circuit, consisting a single voltage source  $V_{Th}$  in series with single resistance  $R_{Th}$ .




→ How to Thevenize a given network

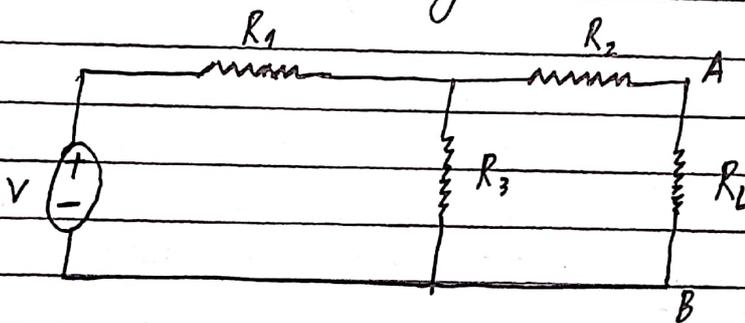

Let us consider a complicated network, we are to find current flowing through  $R_L$  by using Thevenin's Theorem.

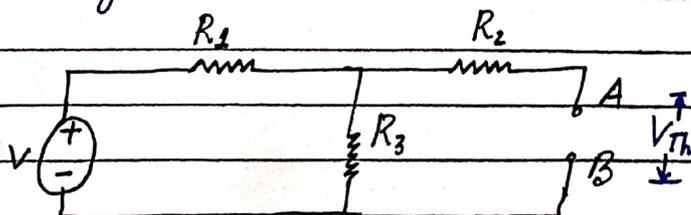
Step 1: Remove the load resistor and calculate the Thevenin's equivalent voltage  $V_{Th}$  across AB



$\therefore V_{Th} = IR_3 = \text{voltage across } R_3$

$$V_{Th} = \frac{V}{R_1 + R_3} \cdot R_3$$

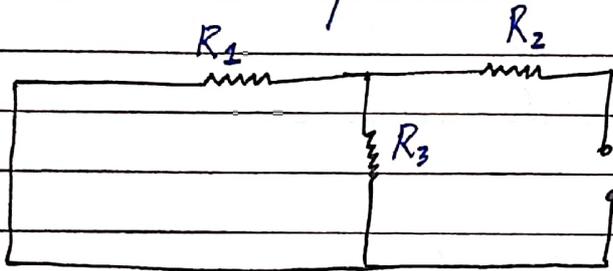
Step 2: Calculate  $R_{Th}$  by voltage source shorted and current source open.



$$R_{Th} = (R_1 \parallel R_3) + R_2$$

$$R_{Th} = \frac{R_1 R_3}{R_1 + R_3} + R_2 \Omega$$

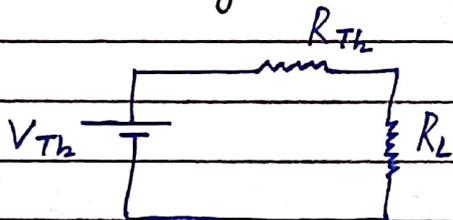
Step 3: Draw the Thevenin's equivalent network by connecting  $V_{Th}$  and  $R_{Th}$  in series.




$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

NOTE:  
Now  $R_L$  is connected back across the terminal AB and find the load current  $I_L$ .

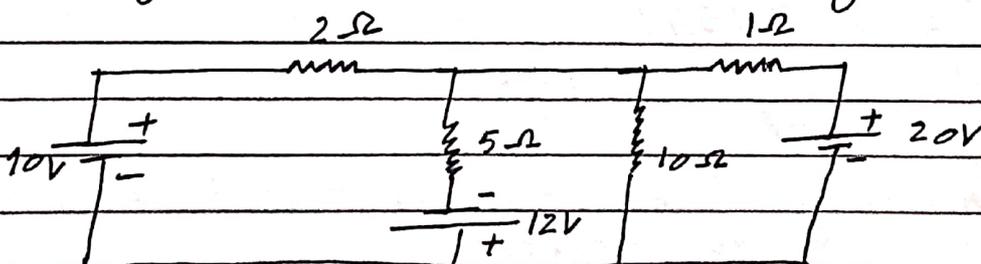Q. Find the current through  $10\Omega$  resistance utilizing Thevenin's theorem of the given network.



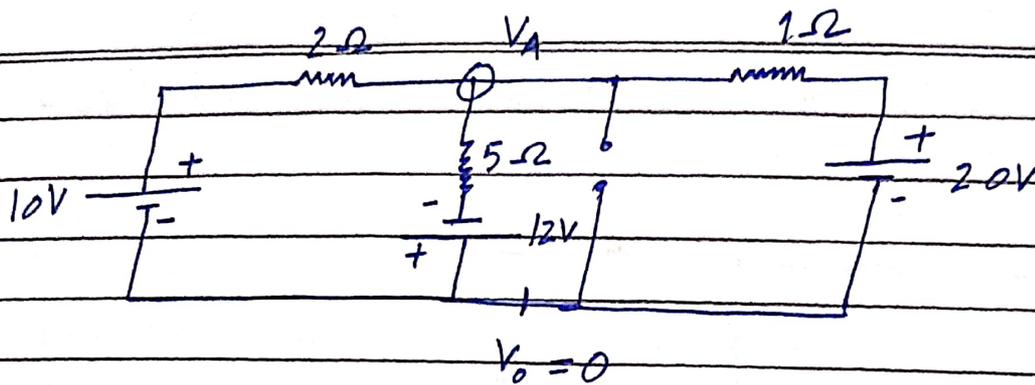Removing  $R_L = 10\Omega$  from the given circuit and calculating  $V_{Th}$ .



∴ Applying KCL at node A


$$\frac{V_A - 10}{2} + \frac{V_A + 12}{5} + \frac{V_A - 20}{1} = 0$$

$$5V_A - 50 + 2V_A + 24 + 10V_A - 200 = 0$$

$$17V_A = 226$$

$$V_A = \frac{226}{17} = 13.29V$$

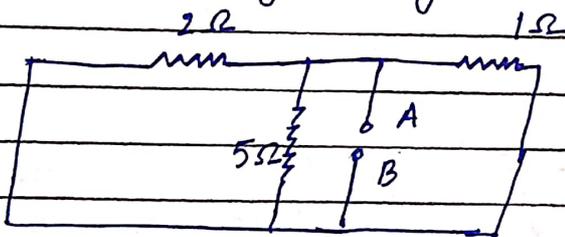→ Now, shorting voltage sources and calculating  $R_{Th}$



$\frac{+}{-}$  → short


$\text{⊖} \rightarrow$  open

$$\therefore R_{Th} = 2 \parallel 5 \parallel 1$$

$$R_{Th} = \frac{10}{17} = 0.588\Omega$$


Now, drawing Thevenin's equivalent circuit:

$$R_{Th} = 0.588\Omega$$

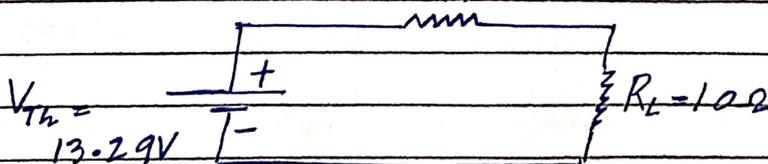


$$\therefore I_L = \frac{13.29}{0.588 + 10} = \frac{13.29}{10.588} = 1.25A \text{ Ans.}$$

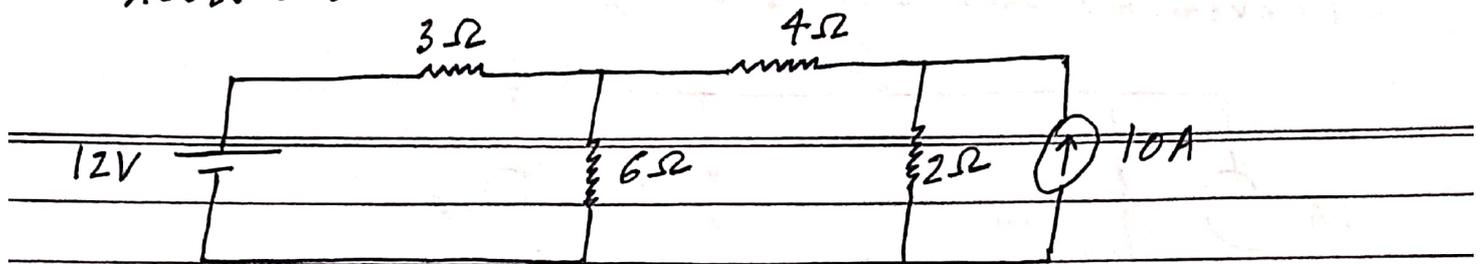Q. Calculate the current flowing through  $4\Omega$  resistor.



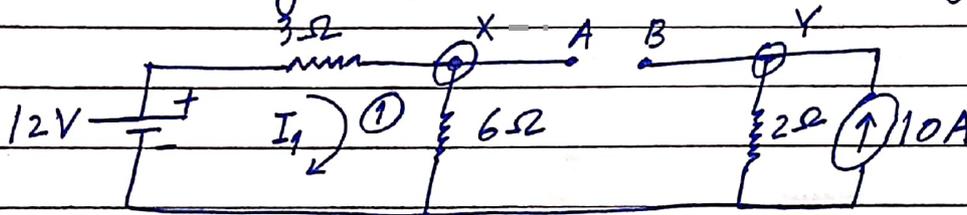Removing  $R_L = 4\Omega$  and calculating  $V_{Th}$ .




$$\therefore I_1 = \frac{12}{3+6} = \frac{12}{9} = \frac{4}{3} \text{ A}$$

$$\therefore \text{Voltage dropped across } 3\Omega = 3 \times \frac{4}{3} = 4\text{V}$$

Hence, voltage on node X =  $12 - 4 = 8\text{V}$   
and voltage on node Y =  $10 \times 2 = 20\text{V}$


$$\Rightarrow V_{AB} = V_{XY} = 20 - 8 = 12\text{V} = V_{Th}$$

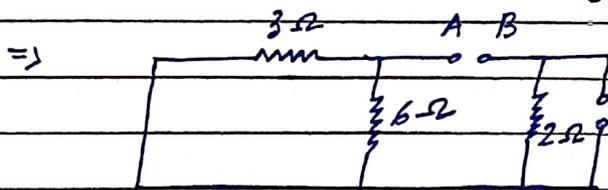Now, shorting voltage sources and opening current sources and calculating  $R_{Th}$ .



$$\therefore R_{Th} = (3 \parallel 6) + 2 = 4\Omega$$

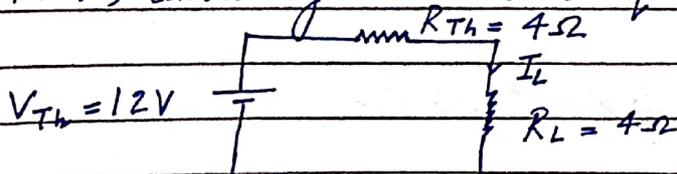
Now, drawing Thevenin's Equivalent circuit:




Hence,

$$I_L = \frac{12}{4+4} = 1.5 \text{ A}$$

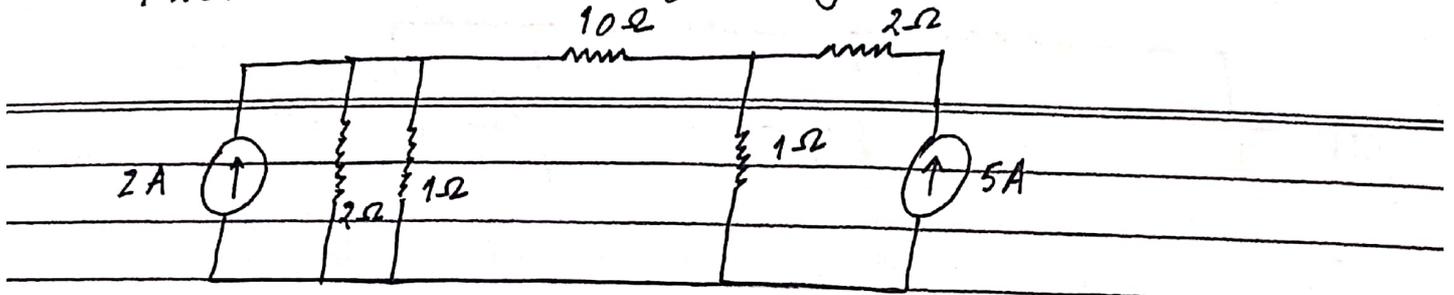
Q. Find the power loss in  $10\Omega$  resistor utilizing Thevenin's theorem of the given circuit.



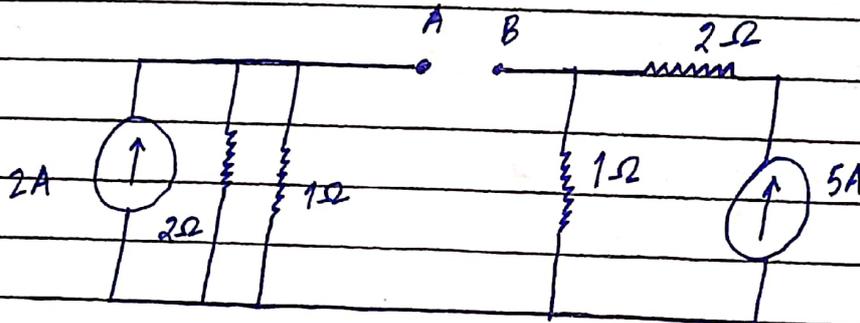Removing  $R_L = 10\Omega$  and calculating  $V_{Th}$ .



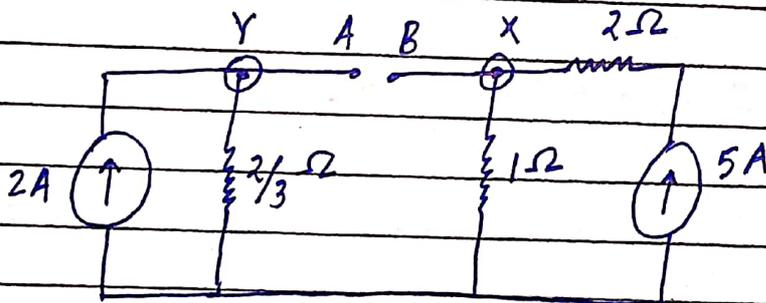$\therefore$  Replacing  $2\Omega$  and  $1\Omega$  with their equivalent resistance of  $\frac{2}{3}\Omega$  (parallel combination).



$\therefore$  Voltage on Y =  $2 \times \frac{2}{3} = \frac{4}{3}V$


$\therefore$  Voltage across  $2\Omega = 5 \times 2 = 10V$   
Voltage across  $1\Omega = 5 \times 1 = 5V$

$\therefore$  Voltage on X =  $10 - 5 = 5V$

Now,

$V_{Th} = V_{AB} = 5 - \frac{4}{3} = \frac{11}{3}V = 3.66V$

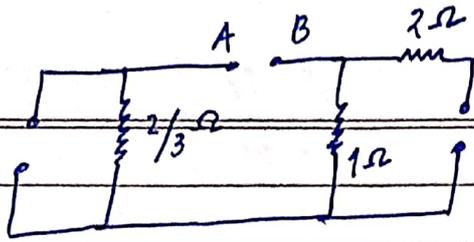
Now, shorting voltage sources and opening current sources, and calculating  $R_{Th}$ .



$$\therefore R_{Th} = 1 + \frac{2}{\frac{2}{3}} = \frac{5}{3} = 1.66 \Omega$$

Now, drawing Thevenin's equivalent circuit.


$$R_{Th} = 1.66 \Omega$$

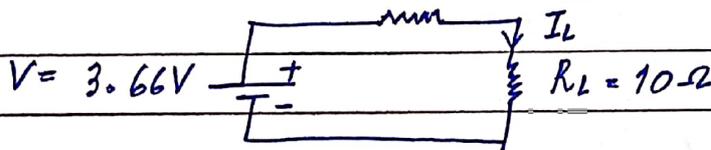

$$\therefore I_L = \frac{3.66}{1.66 + 10} = \frac{3.66}{11.66} = 0.31 A$$

$$\Rightarrow \text{Power dissipated in } 10 \Omega = I^2 R = (0.31)^2 \times 10 = 0.961 W \text{ Ans.}$$


→ Current Divider Rule

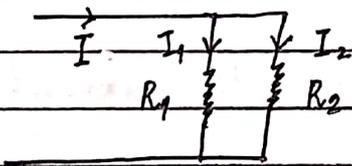

$$I_1 = I_0 \frac{R_2}{R_1 + R_2}$$

$$I_2 = I_0 \frac{R_1}{R_1 + R_2}$$


→ Voltage Divider Rule

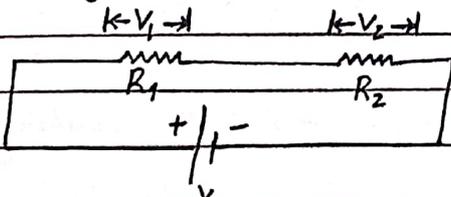

$$V_1 = \frac{R_1 \cdot V}{R_1 + R_2}$$

$$V_2 = \frac{R_2 \cdot V}{R_1 + R_2}$$

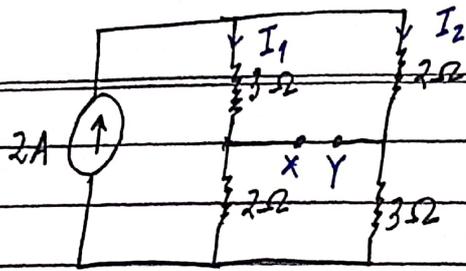Q. Find the Thevenin's equivalent network across the terminal xy on the given terminal.



$I_1 = 1A$   
 $I_2 = 1A$

Because both arms have same resistance, hence current divides equally

$$\Rightarrow V_x = 3 \times I_1 = 3V$$


$$V_y = 2 \times I_2 = 2V$$

$$\therefore V_{xy} = 3 - 2 = 1V = V_{Th}$$

and  $R_{Th} = (3 \parallel 2) + (3 \parallel 2)$


$$= \frac{6}{5} + \frac{6}{5} = \frac{12}{5} = 2.5\Omega$$

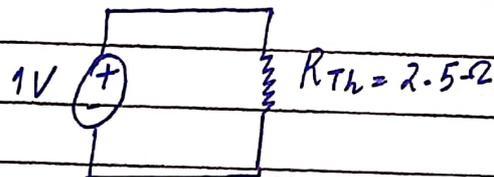$\therefore$  Drawing Thevenin's equivalent network




Ans.

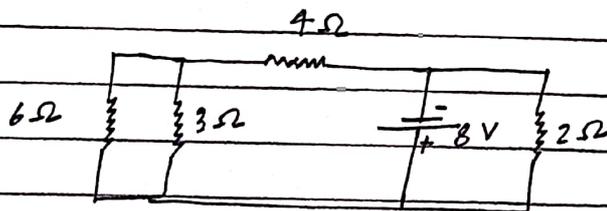Q. Using Thevenin's Theorem, calculate the current through  $3\Omega$  resistor.



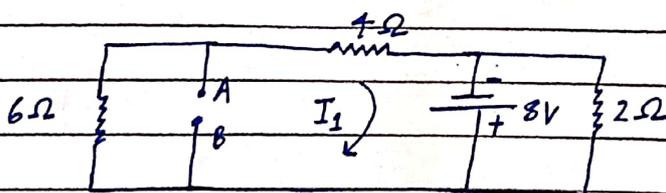Removing the load resistor  $R_L = 3\Omega$  and calculating  $V_{Th}$ .



6004.0

∴ Calculating  $I_1$  from mesh 1


$$10I_1 = 8$$

$$I_1 = 0.8A$$

∴ Voltage across  $6\Omega = 6 \times 0.8 = 4.8V$


This is equal to the voltage across AB i.e.  $V_{th}$  as AB is parallel to  $6\Omega$ .

Now, calculating  $R_{th}$

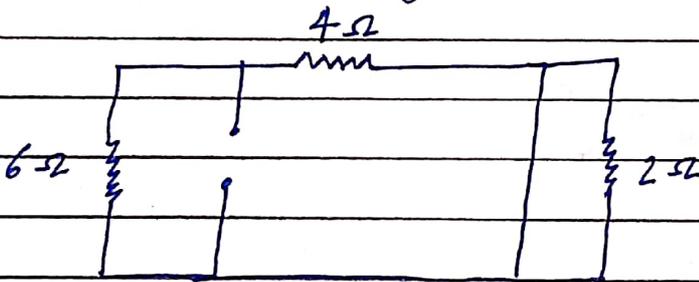

$$\begin{aligned} \therefore R_{th} &= (6 \parallel 4) + 2 \\ &= (2.4\Omega) + 2\Omega \\ &= 4.4\Omega \end{aligned}$$

Drawing Thevenin's Equivalent circuit

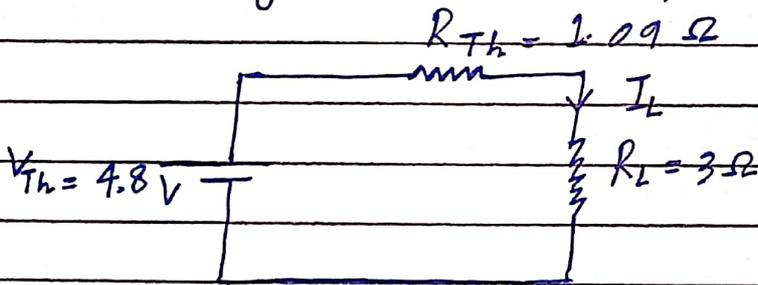

~~How to solve this problem~~


$$\Rightarrow I_L = \frac{4.8}{4.4 + 3} = 1.173A$$

Ans.

इस सवाल में गड़बड़ हो सकती है।

बेहतर है कि आप देरन ले सक एक बार।

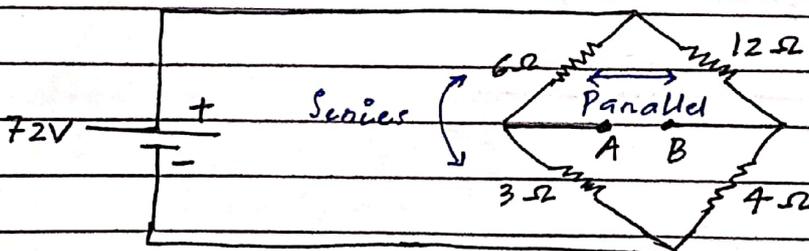Q. Find the Thevenin's equivalent network across the terminal AB after given network;




Applying voltage divider for  $6\Omega$  resistor

$$\therefore V_{6\Omega} = \frac{6 \times 72}{6+3} = 48V \quad \left( \begin{array}{l} 6 \text{ and } 3\Omega \\ \text{resistors} \\ \text{are in series} \end{array} \right)$$

Similarly for  $12\Omega$  resistor

$$\therefore V_{12} = \frac{12 \times 72}{12+4} = 54V \quad \left( \begin{array}{l} 12 \text{ and } 4\Omega \\ \text{resistors are in} \\ \text{series} \end{array} \right)$$

Now;

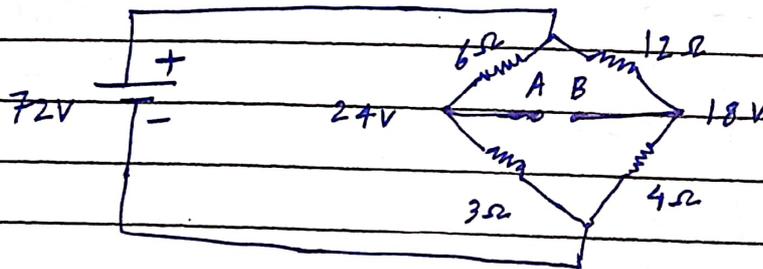


$$\therefore V_A = 72 - 48 = 24V$$

$$V_B = 72 - 54 = 18V$$

$$\therefore V_{Th} = V_A - V_B = 24 - 18 = 6V$$


Now, calculating  $R_{Th}$

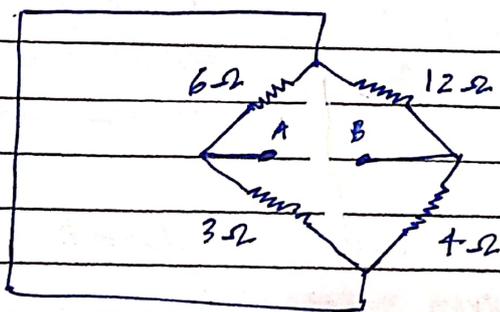

$$R_{Th} = (6 \parallel 12) + (3 \parallel 4)$$
$$= 4 + 12/7$$



$$R_{Th} = 40/7 \Omega = 5.71\Omega$$

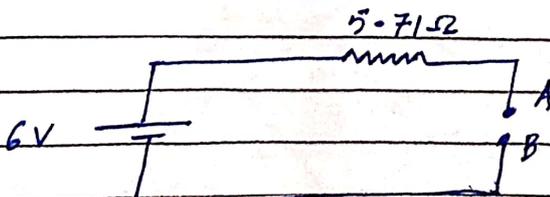$\therefore$  Thevenin's Equivalent Network;



Ans.

## # Norton's Theorem

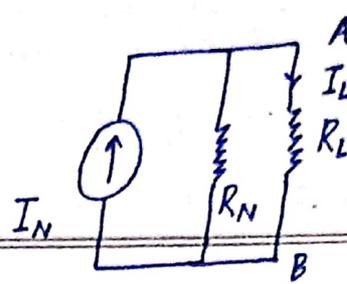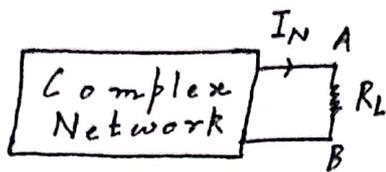


$$I_L = \frac{R_N I_N}{R_N + R_L}$$

Norton equivalent circuit.


→ Norton Theorem is an alternative theorem to the Thevenin's theorem and applicable for a complex network. By using this theorem we can replace a complex network by a current in parallel with a single resistor.

Any linear bilateral network having a terminal A and B can be replaced by single current source  $I_N$  in parallel with a single resistor  $R_L$ .

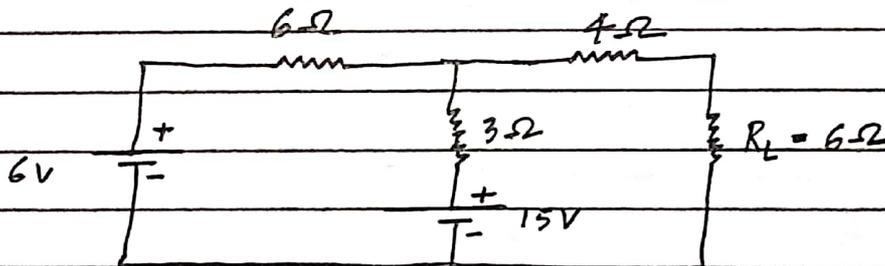Q. Find the current across  $R_L = 6\Omega$ , using Norton's Theorem.



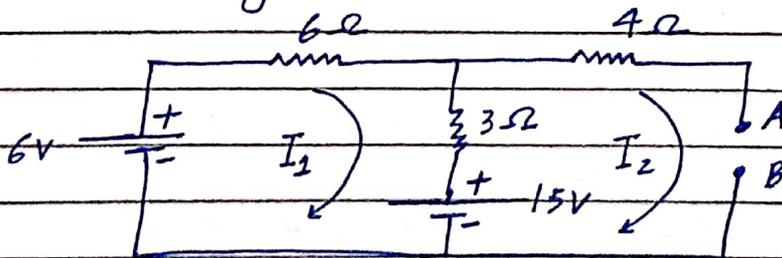Removing  $R_L = 6\Omega$  and calculating  $I_N$



Applying KVL in mesh ①

$$+6 - 6I_1 - 3(I_1 - I_2) - 15 = 0$$

$$-9I_1 + 3I_2 = 9 \quad \text{--- ①}$$

Applying KVL in mesh (2)

$$15 - 3(I_2 - I_1) - 4I_2 = 0$$

$$-7I_2 + 3I_1 = -15 \quad \text{--- (2)}$$

Solving (1) and (2)

$$-9I_1 + 3I_2 = 9$$

$$9I_1 - 2I_2 = -45$$

$$+ \quad + \quad +$$


$$-18I_2 = -36$$

$$I_2 = \frac{36}{18} = 2A$$

And;

$$I_2 = I_N = 2A$$


Now, calculating  $R_N$ ;

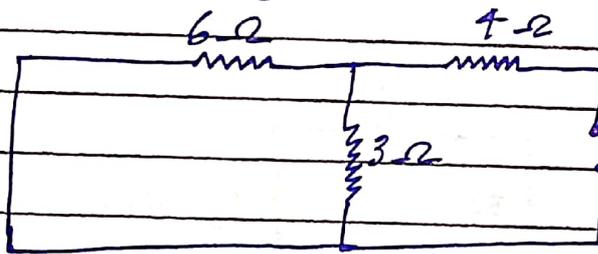

$$\therefore R_N = (6 \parallel 3) + 4$$
$$= \frac{18}{3} + 4$$

$$R_N = 6 \Omega \text{ Ans.}$$


Drawing, Norton's equivalent circuit:

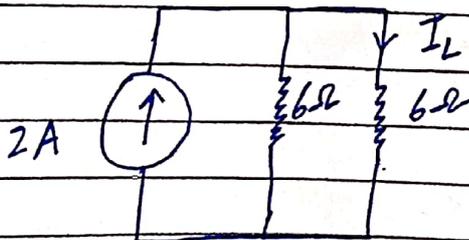


$$I_L = \frac{I_N R_N}{R_L + R_N}$$

$$I_L = \frac{6 \times 2}{12} = 1A \text{ ans.}$$

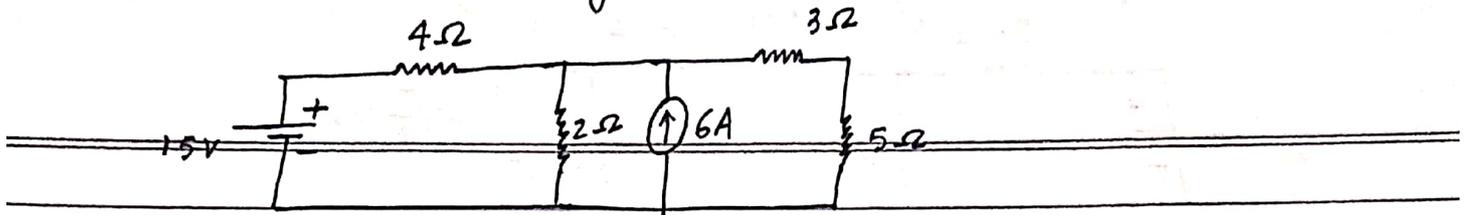Q. Determine the current through  $5\Omega$  resistor using Norton Theorem in given network.



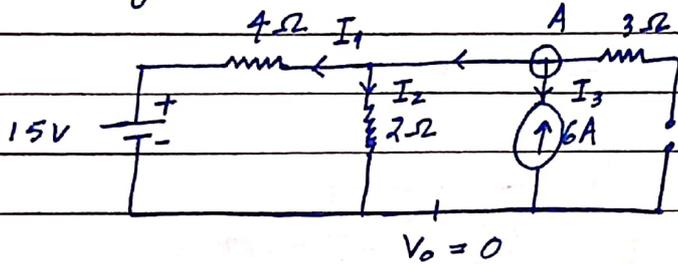Removing  $R_L = 5\Omega$  and calculating  $I_N$



Applying Nodal Analysis at 'A'


∴ Assuming  $I_1$ ,  $I_2$  and  $I_3$  as outgoing current from node A.

⇒ Applying KCL.

$$\therefore \frac{V_A - 15}{4} + \frac{V_A}{2} - 6 = 0$$

$$\therefore \boxed{V_A = 13V} = V_N$$

Now, calculating  $R_N$

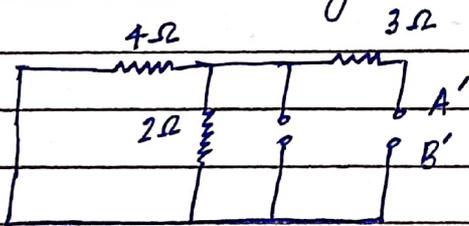


$$R_N = (4/2) + 3$$

$$R_N = 4/3 + 3 = \frac{13}{3} \Omega$$

$$\therefore I_N = \frac{V_N}{R_N} = \frac{13 \times 3}{13} = 3A$$

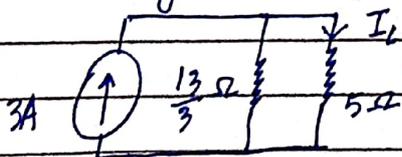
Now, drawing Norton's equivalent circuit;




$$\Rightarrow I_L = \frac{R_N I_N}{R_N + R_L} = \frac{\frac{13}{3} \times 3}{\frac{13}{3} + 5} = 1.39A$$

Ans.

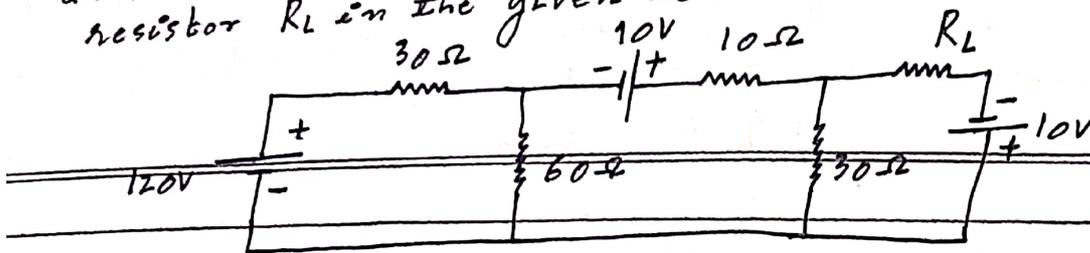Q. Find the Norton equivalent network across the resistor  $R_L$  in the given network.



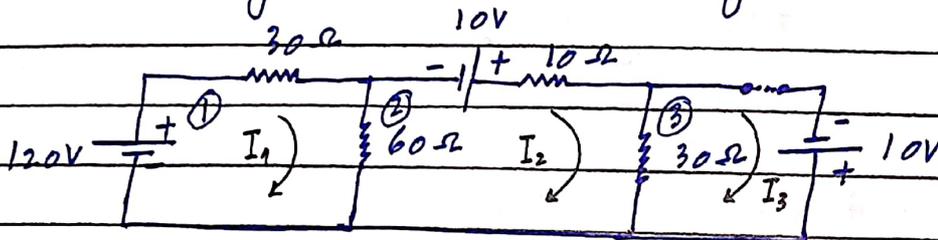Removing  $R_L$  and calculating  $I_N$ ;



∴ KVL for mesh ①

$$120 - 30I_1 - 60I_1 + 60I_2 = 0$$

$$-90I_1 + 60I_2 = -120$$

$$-3I_1 + 2I_2 = -4 \quad \text{--- ①}$$

KVL for mesh ②

$$-60I_2 + 60I_1 + 10 - 10I_2 - 30I_2 + 30I_3 = 0$$

$$-100I_2 + 60I_1 + 30I_3 = -10$$

$$6I_1 - 10I_2 + 3I_3 = -1 \quad \text{--- ②}$$

KVL for mesh ③

$$-30I_3 + 30I_2 + 10 = 0$$

$$3I_2 - 3I_3 = -1 \quad \text{--- ③}$$

Arranging mesh equations into matrix form and using Cramer's rule.

$$\begin{bmatrix} -3 & 2 & 0 \\ 6 & -10 & 3 \\ 0 & 3 & -3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -4 \\ -1 \\ -1 \end{bmatrix}$$

$$\therefore \Delta = -3(30 - 9) - 2(-18)$$

$$= -3(21) + 36$$

$$= -63 + 36$$

$$\Delta = -27$$

$$\Delta_3 = \begin{vmatrix} -3 & 2 & -4 \\ 6 & -10 & -1 \\ 0 & 3 & -1 \end{vmatrix}$$

$$= -3(10+3) - 2(-6) - 4(18)$$


$$= -39 + 12 - 72$$

$$\Delta_3 = -99$$



$$\therefore I_3 = \frac{\Delta_3}{\Delta} = \frac{-99}{-27} = \frac{11}{3} = 3.66 \text{ A} \quad \text{Ans.}$$

$$\Rightarrow I_N = 3.66 \text{ A}$$

Now, calculating  $R_{Th}$

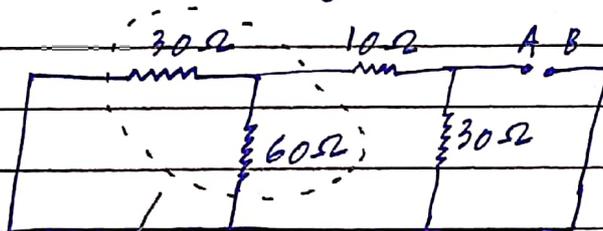

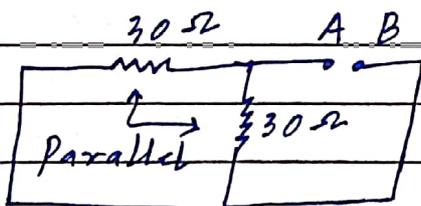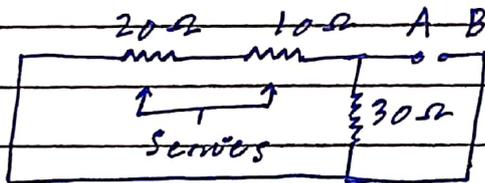
Parallel combination  
 $R_{eq} = 20 \Omega$




$$\Rightarrow R_N = 15 \Omega$$

$$R_{eq} = \frac{30 \times 30}{60} = 15 \Omega$$

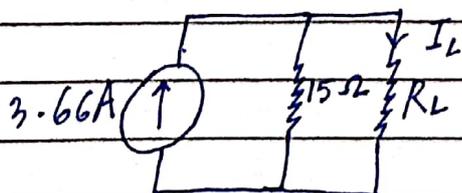
Now, drawing Norton's equivalent Network:



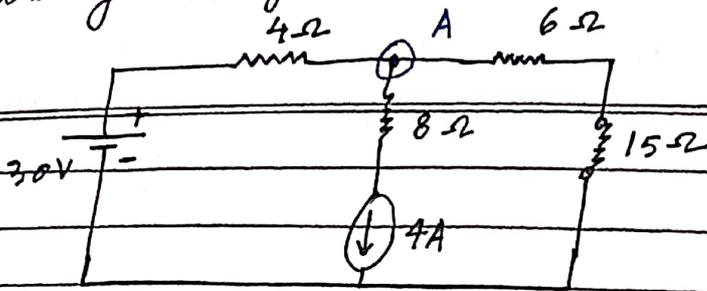Q. Using Norton Theorem, evaluate the current flowing through  $15\ \Omega$  resistor.



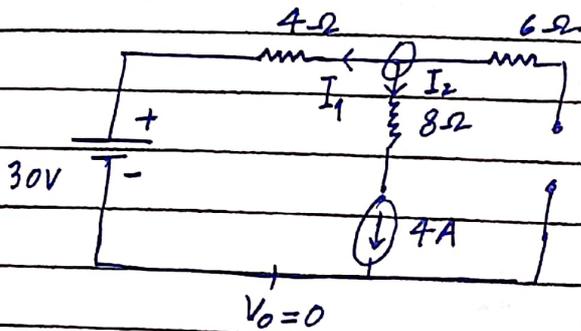Removing  $R_L = 15\ \Omega$  and applying KCL at 'A'




$$\therefore \frac{V_A - 30}{4} + 4 = 0$$

$$V_A - 30 = -16$$

$$V_A = 14\text{V} = V_{Th}$$


Now, calculating  $R_N$ :

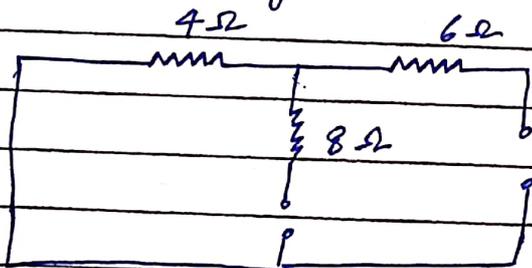

$$R_N = 4 + 6 = 10\ \Omega$$

$$\Rightarrow I_N = \frac{V_N}{R_N} = \frac{14}{10} = 1.4\text{A}$$

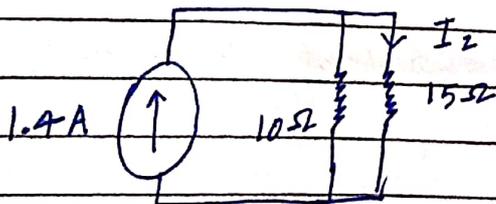Drawing: Norton's equivalent circuit  $\Rightarrow$




$$\therefore I_2 = \frac{1.4 \times 10}{10 + 15} = \frac{14}{25} = 0.55\text{A}$$

Ans.


## # Superposition Theorem

This theorem finds use in solving a network where two or more sources are present and not connected in series or parallel.

In a linear bilateral network containing several energy sources, the overall current in any branch is equal to the algebraic sum of current produced by each source acting alone while the other sources are inactive.

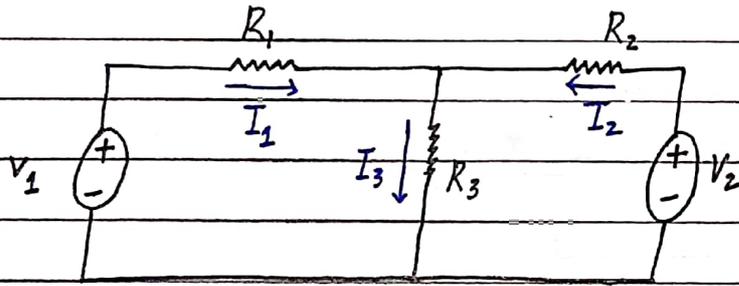

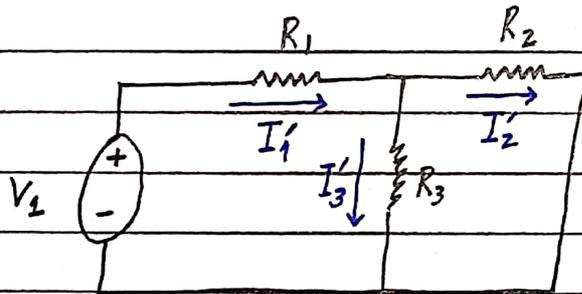Case 1: When  $V_1 \neq 0$ ,  $V_2 = 0$  (inactive)



Consider a complicated network having two voltage sources  $V_1$  and  $V_2$ . Let us calculate the current in each branch using superposition.

According to superposition theorem, select a single source in the given network that means  $V_1 \neq 0$  and  $V_2 = 0$  (short circuited).

$$R_{eq} = \frac{R_2 \cdot R_3}{R_2 + R_3} + R_1$$


$$\therefore I'_1 = \frac{V_1}{\left( \frac{R_2 \cdot R_3}{R_2 + R_3} + R_1 \right)}$$

and using current divider rule,

$$I_2' = \frac{I_1' R_3}{R_2 + R_3}$$

$$I_3' = \frac{I_1' R_2}{R_2 + R_3}$$

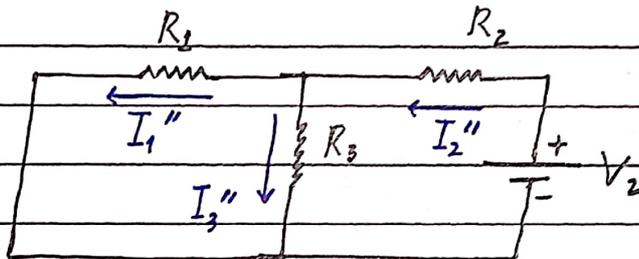Case 2: When  $V_2 \neq 0$ ,  $V_1 = 0$  (in active)



$$R_{net} = (R_1 \parallel R_3) + R_2$$
$$= \left( \frac{R_1 R_3}{R_1 + R_3} + R_2 \right)$$

$$I_2'' = \frac{V_2}{R_{net}}$$

$$\text{and } I_1'' = \frac{R_3}{R_1 + R_3} \times I_2''$$

$$I_3'' = \frac{R_1}{R_1 + R_3} \times I_2''$$


$$\text{or } I_3'' = I_2'' - I_1''$$

$$\therefore I_1 = I_1' - I_1''$$


$$I_2 = I_2' - I_2''$$

$$I_3 = I_3' - I_3''$$

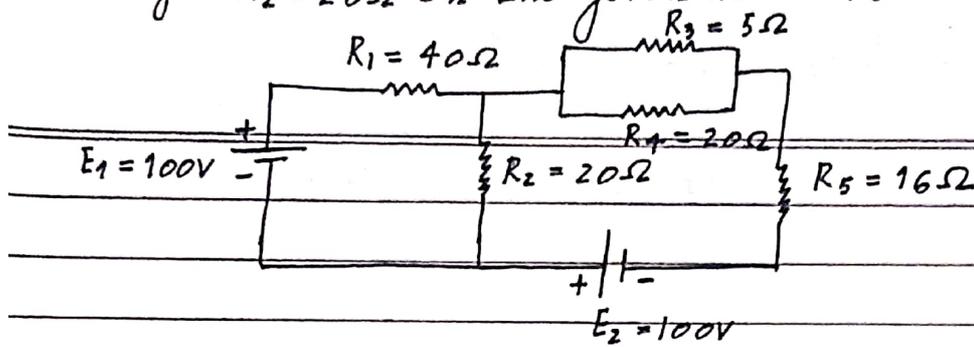Example: Utilising superposition theorem, find the current through  $R_2 = 20\Omega$  in the given network.



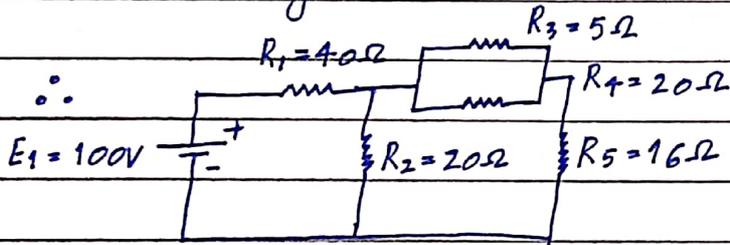Considering  $E_1$  as active source and rest as inactive




$\therefore R_3$  and  $R_4$  are in parallel combination  
 $\Rightarrow R_{eq} = \frac{5 \times 20}{25} \Omega$

and  $R_{eq}$  and  $R_5$  are in series

$$\Rightarrow R'_{eq} = 4 + 16 = 20\Omega$$
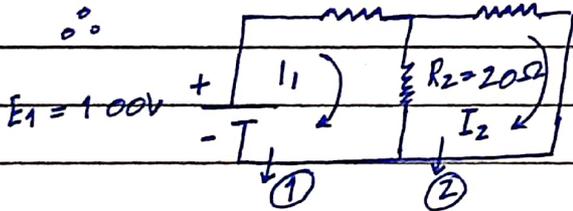
$$R_1 = 40\Omega \quad R'_{eq} = 20\Omega$$



$\therefore$  Applying KVL in mesh ①

$$100 - 40I_1 - 20(I_1 - I_2) = 0$$

$$-60I_1 + 20I_2 = -100$$

$$3I_1 - I_2 = 5 \quad \text{--- ①}$$

Applying KVL in mesh 2

$$-20I_2 - 20(I_2 - I_1) = 0$$

$$-40I_2 + 20I_1 = 0$$


$$I_1 = 2I_2 \quad \text{--- ②}$$

$$\therefore 6I_2 - I_2 = 5 \Rightarrow \boxed{I_2 = 1A} \text{ and } \boxed{I_1 = 2A}$$


Hence,

$$I_{R_2=20\Omega} = I_1 - I_2 = 2 - 1 = 1 \text{ A.}$$

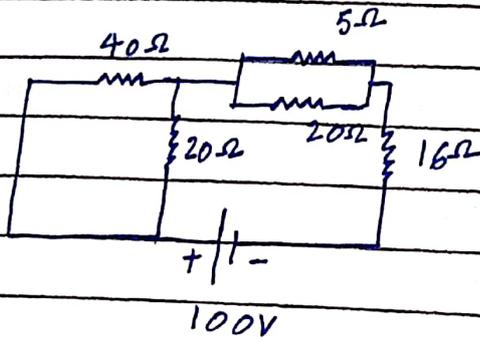Now, considering  $E_2$  as active source and others as inactive sources.



This network can be simplified into;

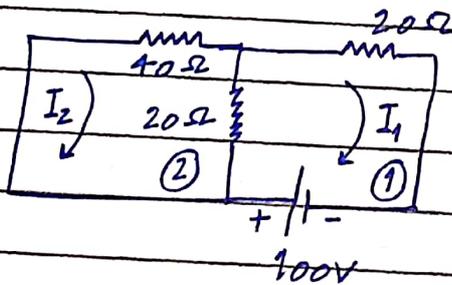

∴ Applying KVL in mesh (1)

$$100 - 20(I_1 - I_2) - 20I_1 = 0$$

$$-40I_1 + 20I_2 = -100$$

$$2I_1 - I_2 = 5 \quad \text{--- (1)}$$

Applying KVL in mesh (2)

$$-40I_2 - 20(I_2 - I_1) = 0$$

$$-60I_2 + 20I_1 = 0$$

$$I_1 = 3I_2 \quad \text{--- (2)}$$


$$\therefore 6I_2 - I_2 = 5$$

$$I_2 = 1 \text{ A}, \quad I_1 = 3 \text{ A}$$

$$\therefore I'_{R_2=20\Omega} = I_1 - I_2 = 3 - 1 = 2 \text{ A}$$



Now, considering 5A as an active source

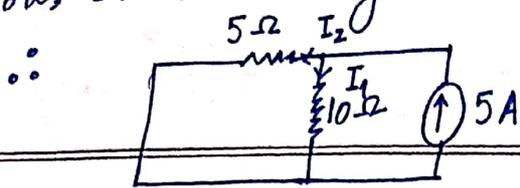

∴ Using Current Divider rule


$$I_1 = \frac{5 \times 5}{15} = \frac{5}{3} \text{ A}$$

$$\Rightarrow V_{10\Omega}'' = 10 \times \frac{5}{3} = \frac{50}{3} \text{ V} = 16.66 \text{ V}$$


∴ Voltage across  $10\Omega$  when both sources are active is

$$\begin{aligned} \Rightarrow V_{10\Omega} &= V_{10\Omega}' + V_{10\Omega}'' \\ &= 6.66 + 16.66 \\ V_{10\Omega} &= 23.32 \text{ V} \text{ Ans.} \end{aligned}$$

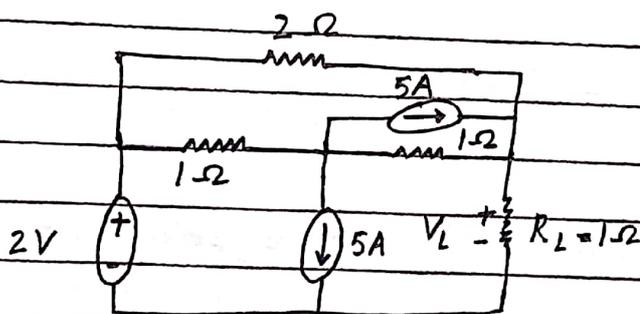Q. Find the voltage  $V_L$  in the given network using superposition theorem.



Considering 2V as an active source;

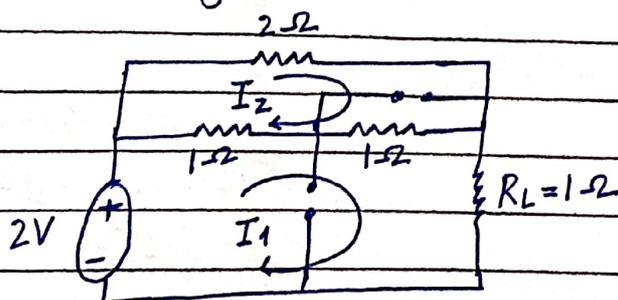

Applying KVL in mesh 1

$$-2(i_1 - i_2) - i_1 + 2 = 0$$

$$-3i_1 + 2i_2 = -2 \quad \text{--- (1)}$$

Applying KVL in mesh 2

$$-2(i_2 - i_1) - 2i_2 = 0$$

$$-4i_2 + 2i_1 = 0$$

$$4i_2 = 2i_1$$

$$i_1 = 2i_2 \quad \text{--- (2)}$$

Putting (2) in (1)


$$-6i_2 + 2i_2 = -2$$

$$-4i_2 = -2$$

$i_2 = 0.5 \text{ A}$
$i_1 = 1 \text{ A}$


∴  $V_L' = 1 \text{ V}$

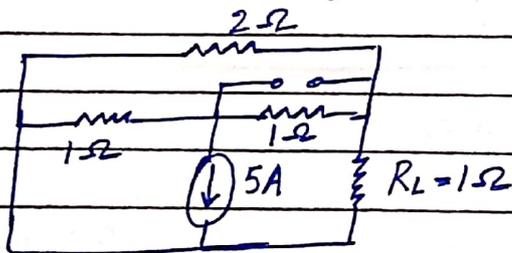Now, considering '5A' as an active source



∴  $V_L'' = 5 \times 1 = 5 \text{ V}$

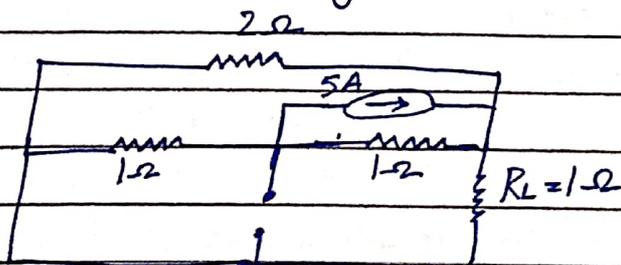Now, considering '5A' as an active source



∴  $V_L''' = 5 \times 1 = 5 \text{ V}$



Hence  $V_L = V_L' + V_L'' + V_L'''$

$$V_L = 1 + 5 + 5 = 11 \text{ Ans}$$
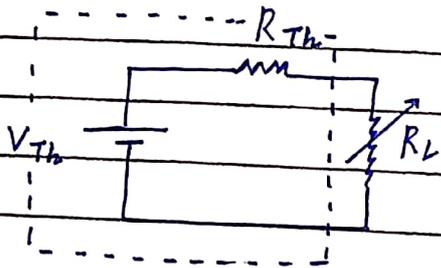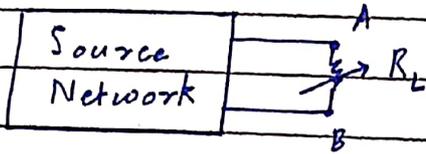
## # Maximum Power Transfer Theorem

Maximum Power Transfer Theorem deals with power from a source to load. This theorem is used to find the value of load resistance for which there would be maximum amount of power from source to load.

A load resistance, being connected to a DC network receives maximum power when the load resistance is equal to the internal resistance of the source network.



$$R_L = R_{Th}$$

Maximum power delivered.

$$P = I_L^2 \cdot R_L$$

$$P = \frac{V_{Th}^2}{(R_{Th} + R_L)^2} \cdot R_L$$

$$P = \frac{V_{Th}^2}{(2R_L)^2} \cdot R_L$$

$$P_{max} = \frac{V_{Th}^2}{4R_L}$$

This theorem states that maximum power from a complex network is obtained when the load resistance

$R_L$  is equivalent to Thevenin's equivalent resistance  $R_{Th}$

as seen from the load terminals.

Consider a variable resistance  $R_L$  is connected to DC source network having  $V_{Th}$  (Thevenin's equivalent voltage) and Thevenin's equivalent resistance  $R_{Th}$  of the source network.

Therefore, we know that  $V_{Th} = I_L (R_{Th} + R_L)$  and the power

delivered to load resistor is

$$P = I_L^2 \times R_L$$

$$P = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 \times R_L$$

Power  $P$  can be maximized by varying  $R_L$  when maximum power can be delivered to the load. When

$$P_L(\max) = \frac{dP}{dR_L} = 0$$

$$\therefore \frac{d}{dR_L} \left( \left( \frac{V_{th}}{R_{th} + R_L} \right)^2 \times R_L \right) = 0$$

$$R_L \cdot V_{th}^2 \left( \frac{d(R_{th} + R_L)^{-2}}{dR_L} \right) + \frac{V_{th}^2}{(R_{th} + R_L)^2} = 0$$

$$\frac{R_L \times V_{th}^2 \times (-2)}{(R_{th} + R_L)^3} + \frac{V_{th}^2}{(R_{th} + R_L)^2} = 0$$

$$\therefore -2 \times R_L \times V_{th}^2 = -V_{th}^2 \times R_{th} - V_{th}^2 \cdot R_L$$

$$\Rightarrow \boxed{R_L = R_{Th}}$$

Hence,  $R_L = R_{Th}$ , the system being perfectly matched for load and source. The power transfer becomes maximum and this amount of power is

$$P = \frac{V_{th}^2}{(R_L + R_{Th})^2} \times R_L = \frac{V_{th}^2 \times R_L}{4R_L^2} = \frac{V_{th}^2}{4R_L}$$

→ Efficiency ( $\eta$ ):  $\frac{\text{Output Power}}{\text{Input Power}}$


$$= \frac{I_L^2 \cdot R_L}{I_L^2 (R_{Th} + R_L)} = \frac{R_L}{R_{th} + R_L}$$

Therefore maximum efficiency is


$$P = \frac{R_{Th}}{2R_{Th}} = 0.5 = 50\%$$

NOTE: Efficiency in maximum power transfer is only 50% as one half of the total power generated in internal resistance of the source network.

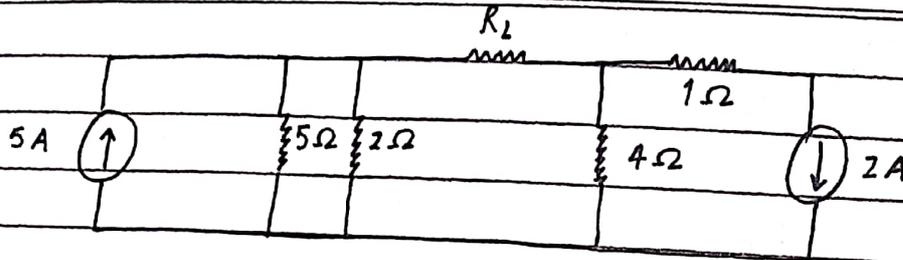Q. Find the value of  $R_L$  such that maximum power transfer takes place from the current sources to the load resistor  $R_L$  and also obtain the amount of maximum power transferred in the given network.



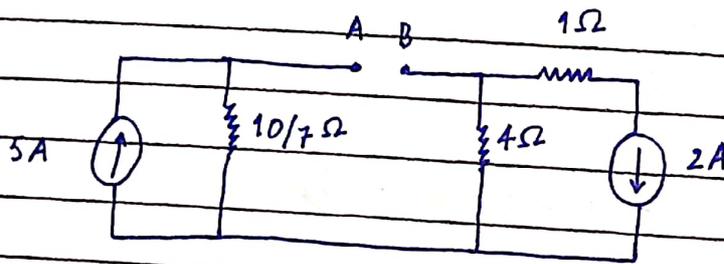Removing load resistance and calculating  $V_{Th}$ .




Replacing  $5\Omega$  and  $2\Omega$  with their eq. resistance.

$$\therefore R_{eq} = (5 \parallel 2) = 10/7 \Omega$$

$$\therefore V_A = 5 \left( \frac{10}{7} \right) = 50 = 7.14V$$


and

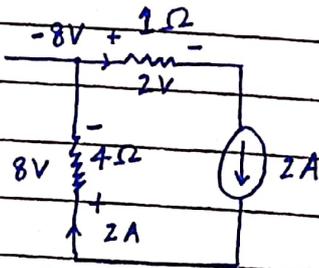

$$\therefore V_B = -8V$$

$$\therefore V_{AB} = (7.14) - (-8) = 15.14V = V_{Th}$$

Now, calculating  $R_{Th}$ ;

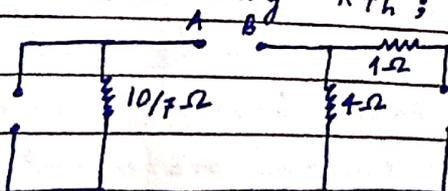


$$\therefore R_{Th} = \frac{10}{7} + 4 = 5.43 \Omega$$

∴ To transfer maximum power;  
 $R_L = R_{th} = 5.43 \Omega$


According to Maximum Power Transfer Theorem;

$$P_{Max} = \frac{V_{th}^2}{4R_L} = \frac{(15.17)^2}{4 \times 5.43} = 10.553 \text{ W} \quad \text{Ans.}$$

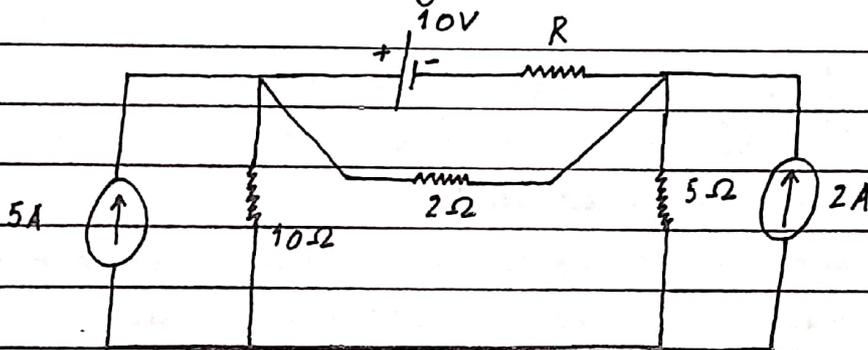Q. Obtain maximum amount of power in the resistor R from the source using maximum power transfer theorem



Removing 'R' and calculating  $V_{th}$

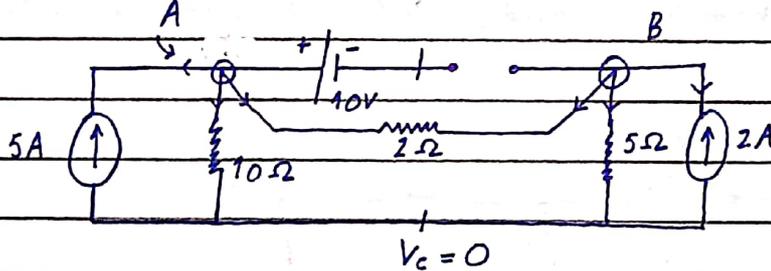

Applying nodal analysis at 'A'

$$-5 + \frac{V_A}{10} + \frac{V_A - V_B}{2} = 0$$

$$6V_A - 5V_B = 50 \quad \text{--- (1)}$$

Applying Nodal Analysis at B

$$\therefore \frac{V_B - 10}{2} + \frac{V_B}{5} - 2 = 0$$

$$7V_B - 5V_A = 20 \quad \text{--- (2)}$$

On solving (1) and (2), we get


$$V_A = 26.46 \text{ V}$$

$$V_B = 21.76 \text{ V}$$

$$\therefore V_{AB} = 26.46 - 21.76 = 5.3 \text{ V} = V_{th}$$

Now, calculating  $R_{Th}$ :


$$R_{Th} = (10 + 5) // 2 = 1.76 \Omega$$

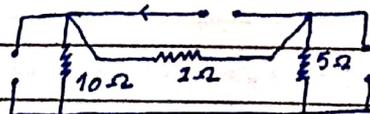

$$\therefore P_{Max} = \frac{V_{th}^2}{4R_L} = \frac{5.3 \times 5.3}{4 \times 1.76 \times 1.76} = 3.990 \approx 4 \text{ W} \quad \text{Ans.}$$
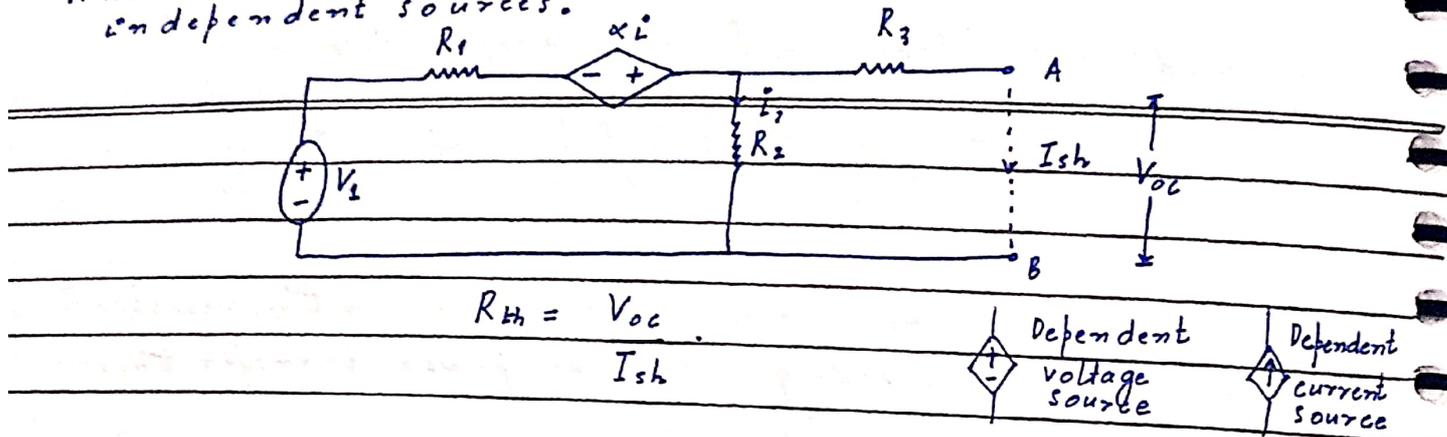
## Dependent Source

When circuit contains both independent and dependent sources.




→ Procedure for finding  $V_{Th}$  and  $R_{Th}$ .

Step 1: Calculate the open circuited voltage  $V_{oc}$  as usual with all sources as activated.

Step 2: A short circuit is applied across the open terminal and find the value of short circuited current.

Step 3: Find Thevenin's equivalent resistance.

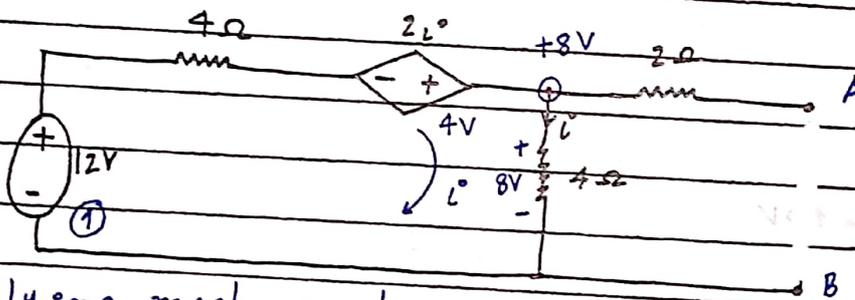Q. Find the Thevenin's equivalent network for the given network.




Applying mesh analysis in ①

$$\therefore 12 - 4i' + 2i' - 4i' = 0$$

$$12 - 6i' = 0$$

$$i' = 2$$

$$\therefore V_{oc} = 8V$$

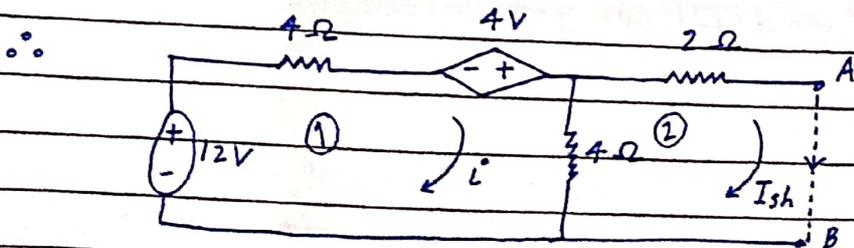

Short-circuiting terminal AB and calculating  $I_{sh}$  by using mesh analysis

∴ Applying mesh analysis in (1)

$$12 - 4i + 4 - 4(i - i_{sh}) = 0$$

$$16 - 8i + 4i_{sh} = 0 \quad \text{--- (1)}$$

Applying mesh analysis in (2)

$$4(i_{sh} - i) + 2i_{sh} = 0$$

$$6i_{sh} = 4i$$

$$3i_{sh} = 2i$$

Putting this in (1)


$$16 - 12i_{sh} + 4i_{sh} = 0$$

$$16 - 8i_{sh} = 0$$

$$i_{sh} = 2 \text{ A}$$

$$\therefore R_{th} = \frac{V_{oc}}{I_{sh}} = \frac{8}{2} = 4 \Omega$$

∴ Thevenin's equivalent network is

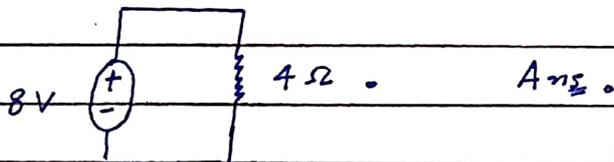

These handwritten notes are of ESC-S101 taught to us by Prof. Om Pal, compiled and organized chapter-wise to help our juniors. We hope they make your prep a bit easier.

— **Saksham Nigam** and **Misbahul Hasan** (B.Tech. CSE(2024-28))